

# EECS 370 - Lecture 12

## Multi-cycle + Introduction to Pipelining



# Announcements

- •P2
- •Three parts: part a is due today
- •HW 2
- •Posted on website, due next Mon
- •Midterm exam Thu 10/9 6-8 pm
- •Sample exams on website
- •You can bring 1 sheet (double sided is fine) of notes
- •We will provide LC2K encodings + ARM cheat sheet
- •Calculator that doesn't connect to internet is recommended
- •Staff led review session on Sunday
- •Will be recorded, see Ed post
- •Lecture on Tuesday will also be review



# What's Wrong with Single-Cycle?

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

What is the latency of lw?

	Get Instr	read reg	ALU oper.	mem	write reg	
• add:	2ns	+ 1ns	+ 2ns		+ 1 ns	= 6 ns
• beq:	2ns	+ 1ns	+ 2ns			= 5 ns
• sw:	2ns	+ 1ns	+ 2ns	+ 2ns		= 7 ns
• lw:	2ns	+ 1ns	+ 2ns	+ 2ns	+ 1ns	= 8 ns



# Review: What's Wrong with Single-Cycle?

- **All instructions run at the speed of the slowest instruction.**
- Adding a long instruction can hurt performance
  - What if you wanted to include multiply?
- You cannot reuse any parts of the processor
  - We have 3 different adders to calculate  $PC+1$ ,  $PC+1+offset$  and the ALU
- No benefit in making the common case fast
  - Since every instruction runs at the slowest instruction speed
    - This is particularly important for loads as we will see later




# Multiple-Cycle Execution

- Each instruction takes multiple cycles to execute
  - Cycle time is reduced
  - Slower instructions take more cycles
  - Faster instructions take fewer cycles
    - We can start next instruction earlier, rather than just waiting
  - Can reuse datapath elements each cycle
- What is needed to make this work?
  - Since you are re-using elements for different purposes, you need more and/or wider MUXes.
  - You may need extra registers if you need to remember an output for 1 or more cycles.
  - Control is more complicated since you need to send new signals on each cycle.




# Multi-cycle LC2 Datapath

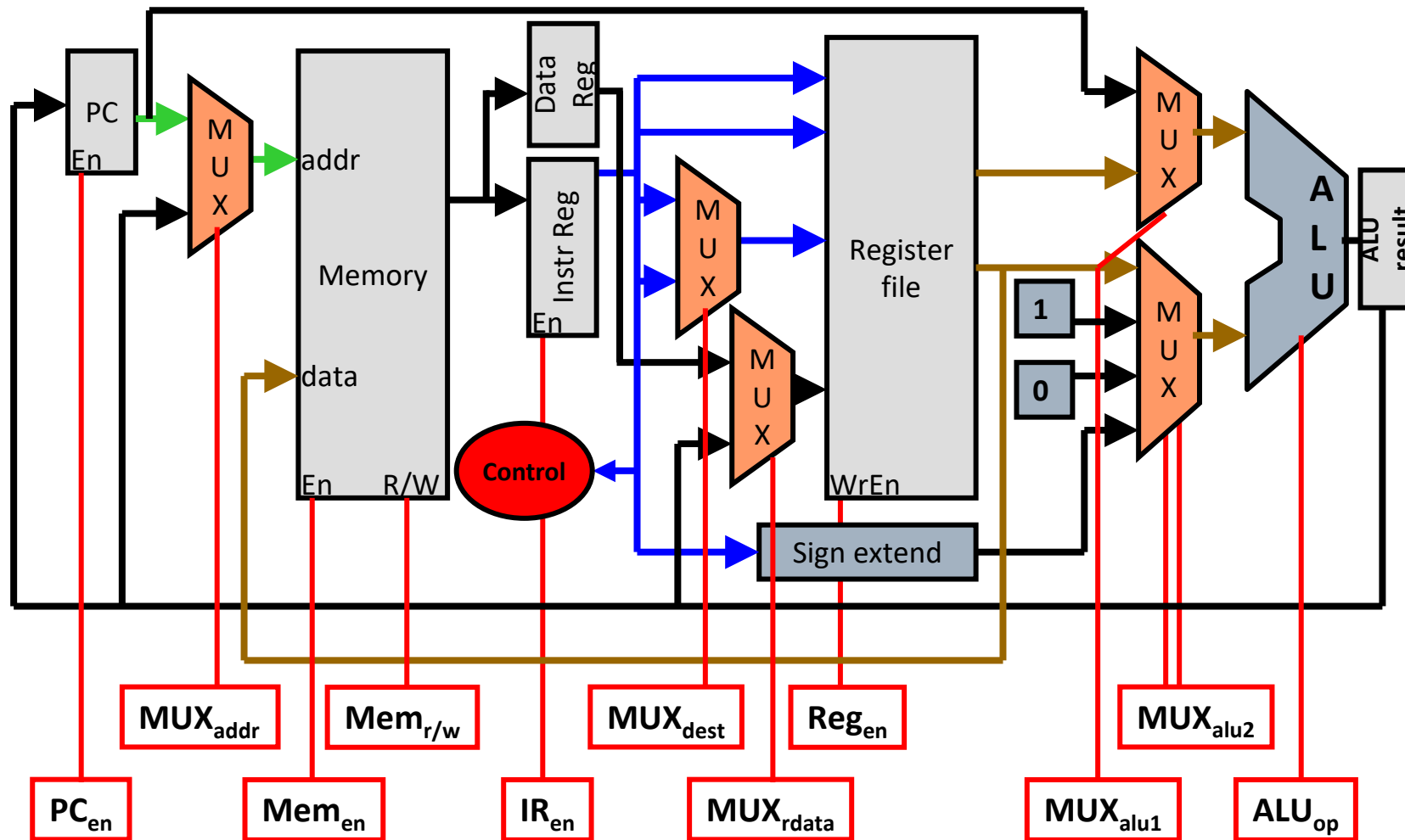


Each red signal comes from "Control"  
(implemented via ROM as before)
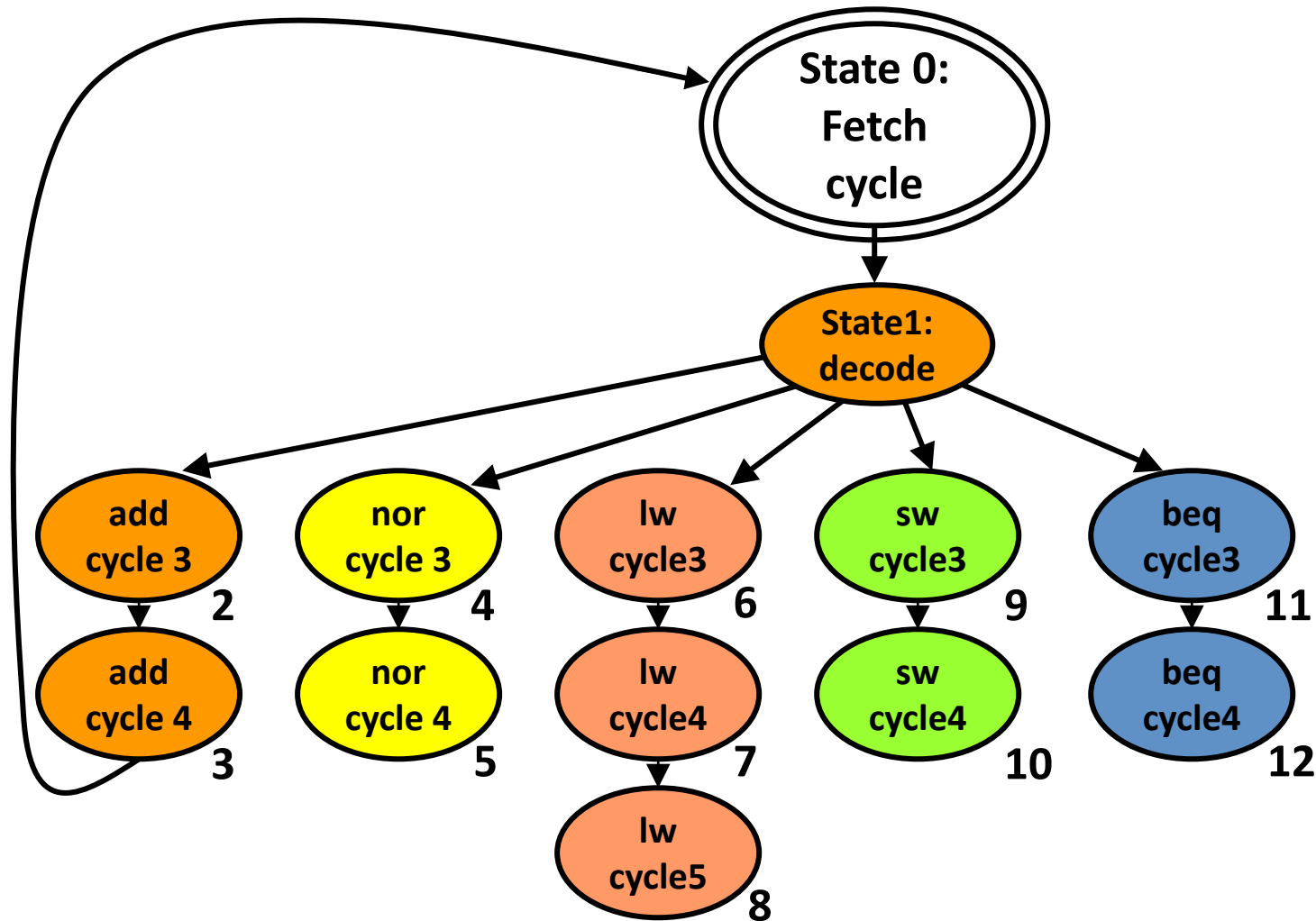
# State machine for multi-cycle control signals (transition functions)




Note: we aren't worrying about JALR instruction in hardware going forward

# Implementing FSM

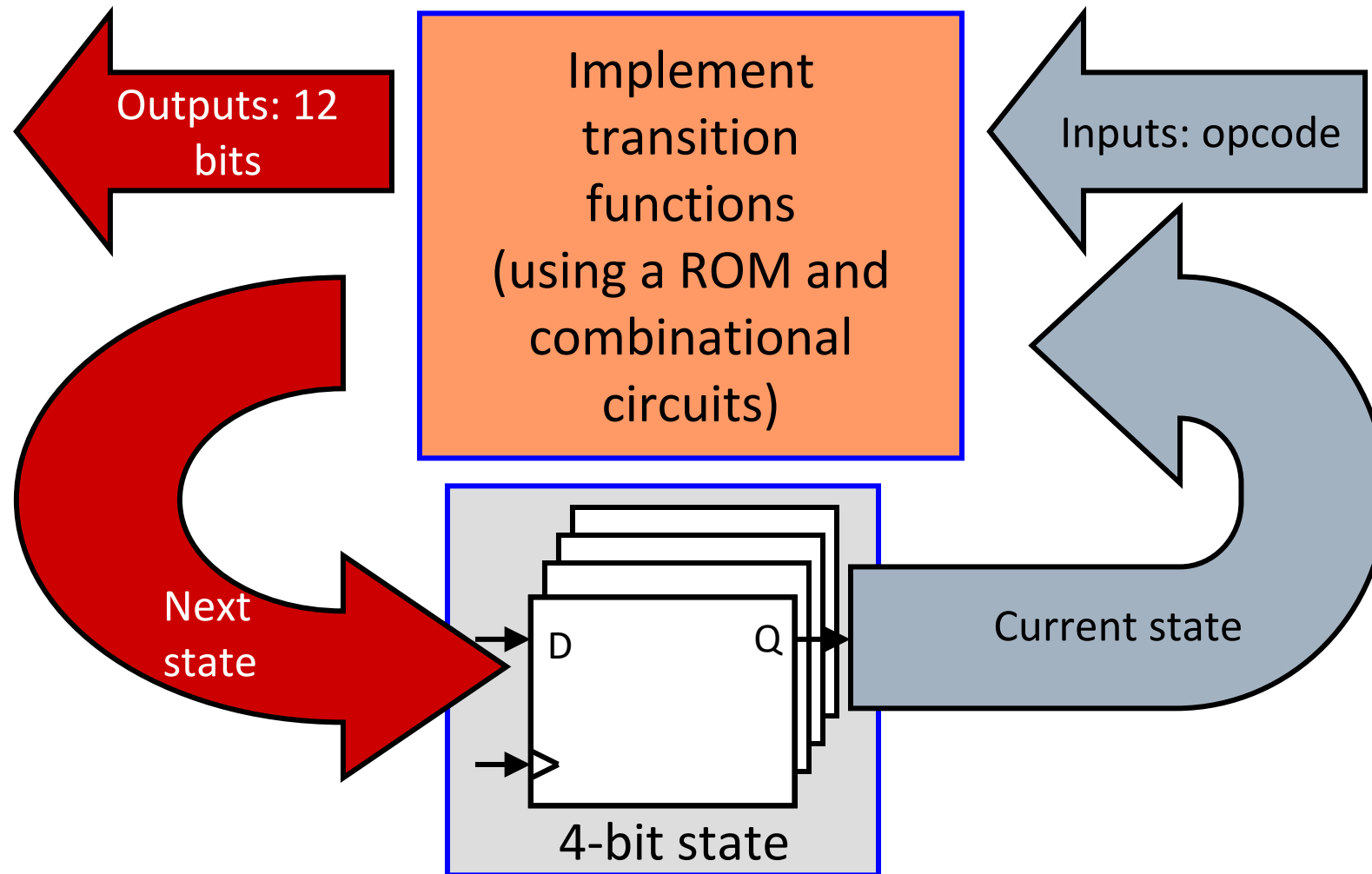




# Building the Control ROM

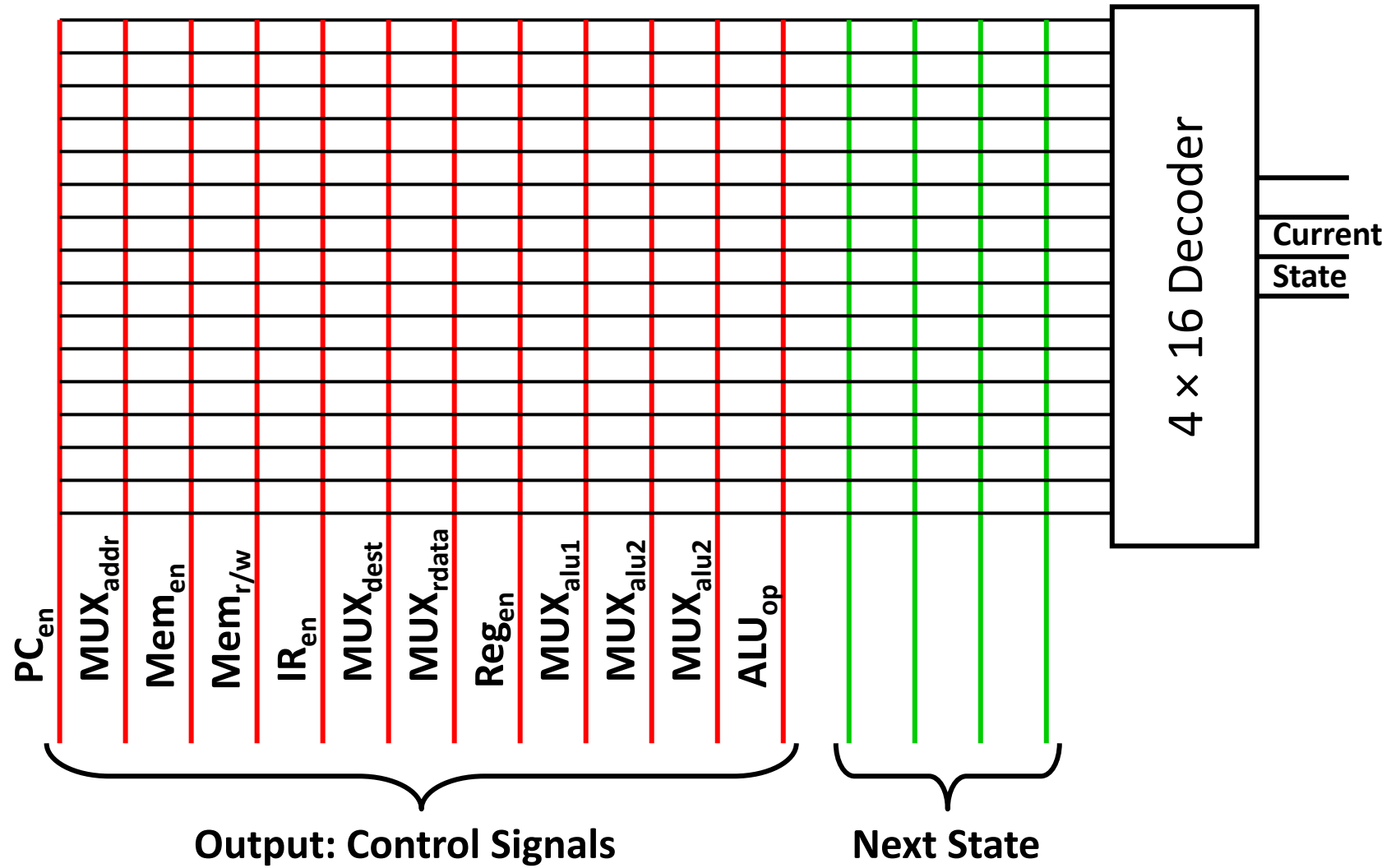

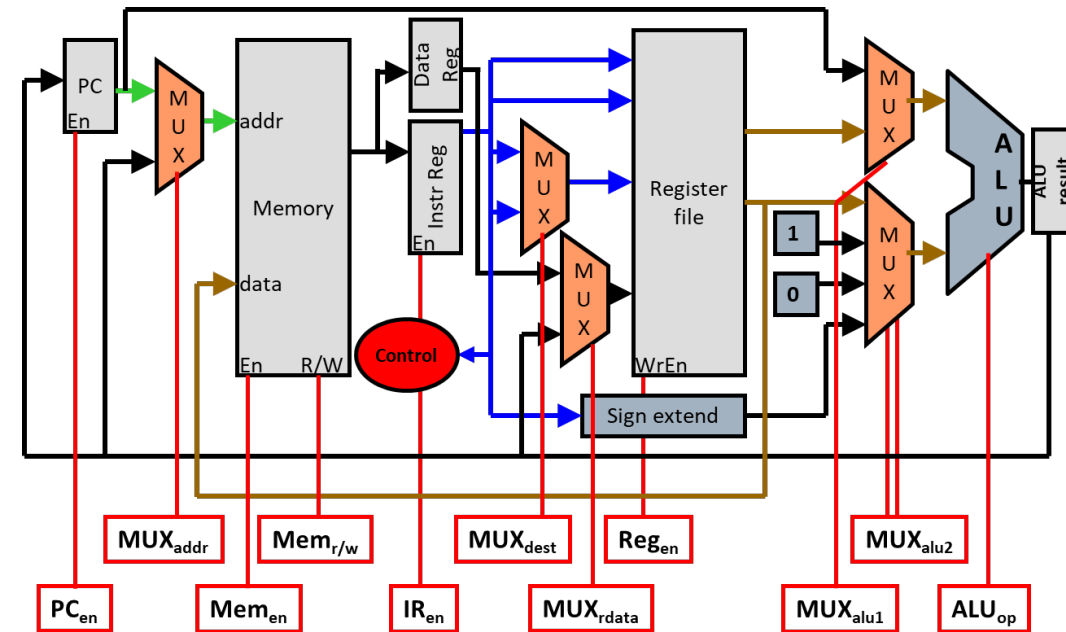
# First Cycle (State 0) Fetch Instr

- What operations need to be done in the first cycle of executing any instruction?
  - Read memory[PC] and store into instruction register.
    - Must select PC in memory address MUX ( $MUX_{addr} = 0$ )
    - Enable memory operation ( $Mem_{en} = 1$ )
    - R/W should be (read) ( $Mem_{r/w} = 0$ )
    - Enable Instruction Register write ( $IR_{en} = 1$ )
  - Calculate PC + 1
    - Send PC to ALU ( $MUX_{alu1} = 0$ )
    - Send 1 to ALU ( $MUX_{alu2} = 01$ )
    - Select ALU add operation ( $ALU_{op} = 0$ )
  - $PC_{en} = 0$ ;  $Reg_{en} = 0$ ;  $MUX_{dest}$  and  $MUX_{rdata} = X$
- Next State: Decode Instruction



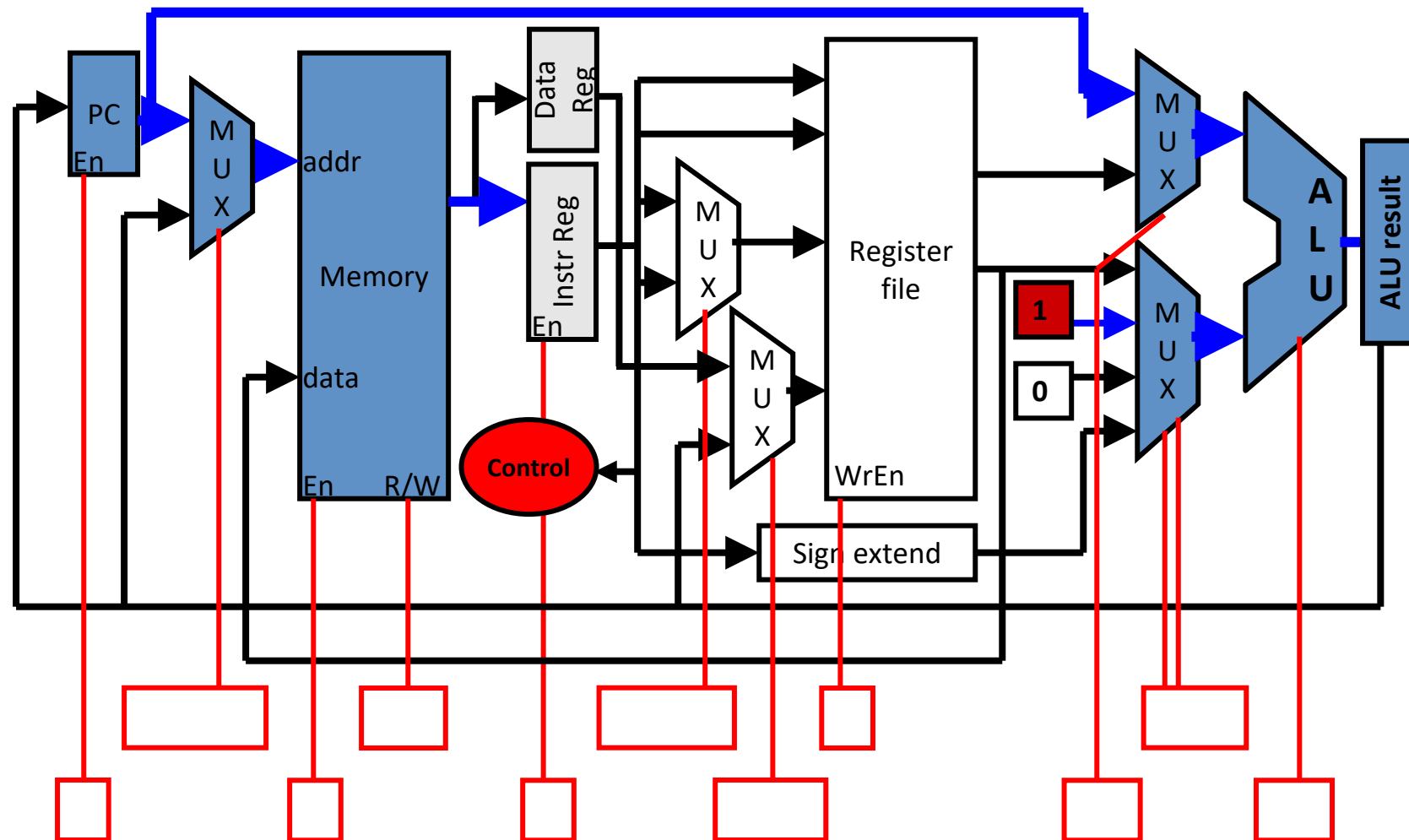
# First Cycle (State 0) Fetch Instr

This is the same for all instructions  
(since we don't know the instruction yet!)



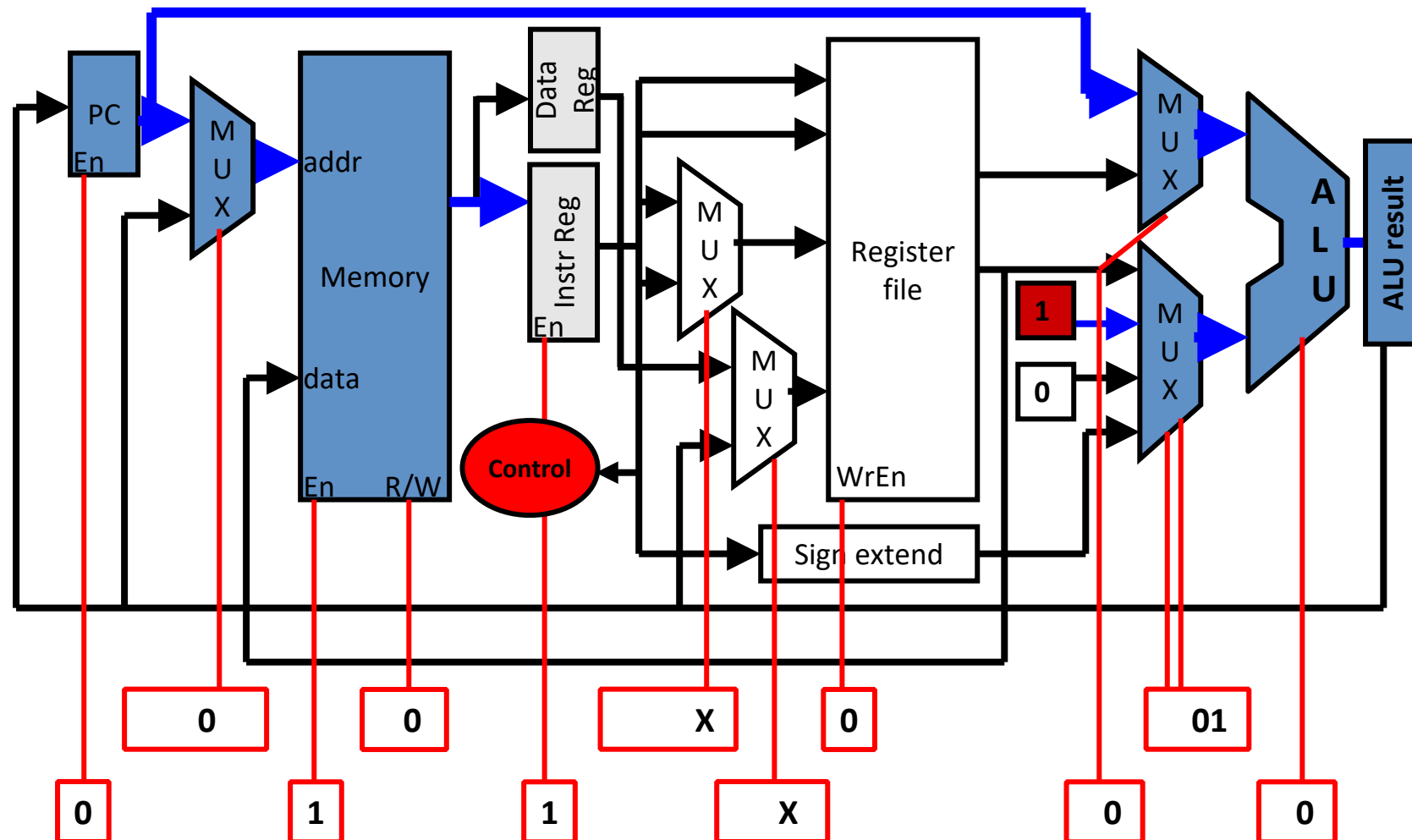
# First Cycle (State 0) Fetch Instr


This is the same for all instructions  
(since we don't know the instruction yet!)



# Building the Control ROM

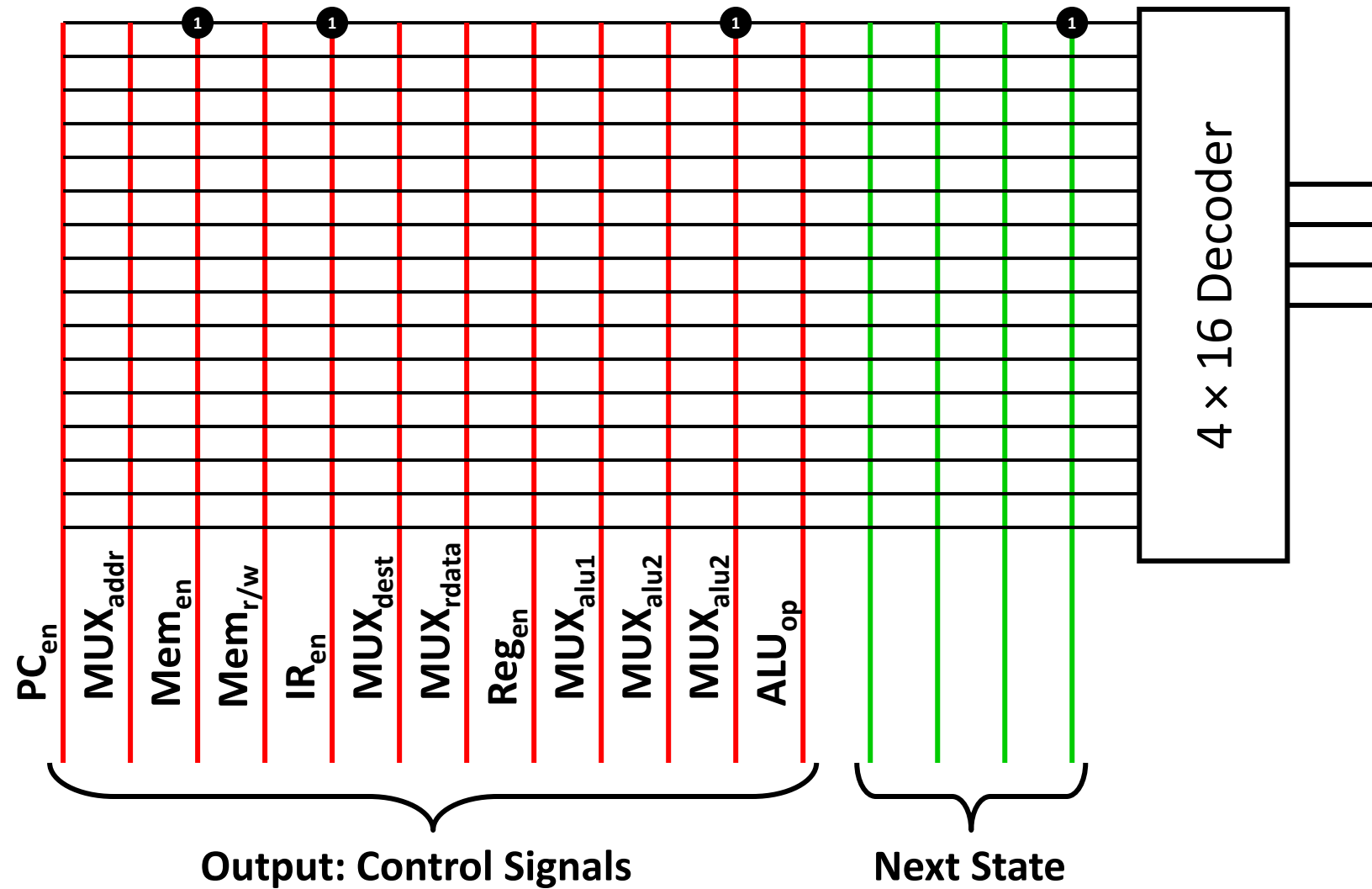

# State 1: instruction decode

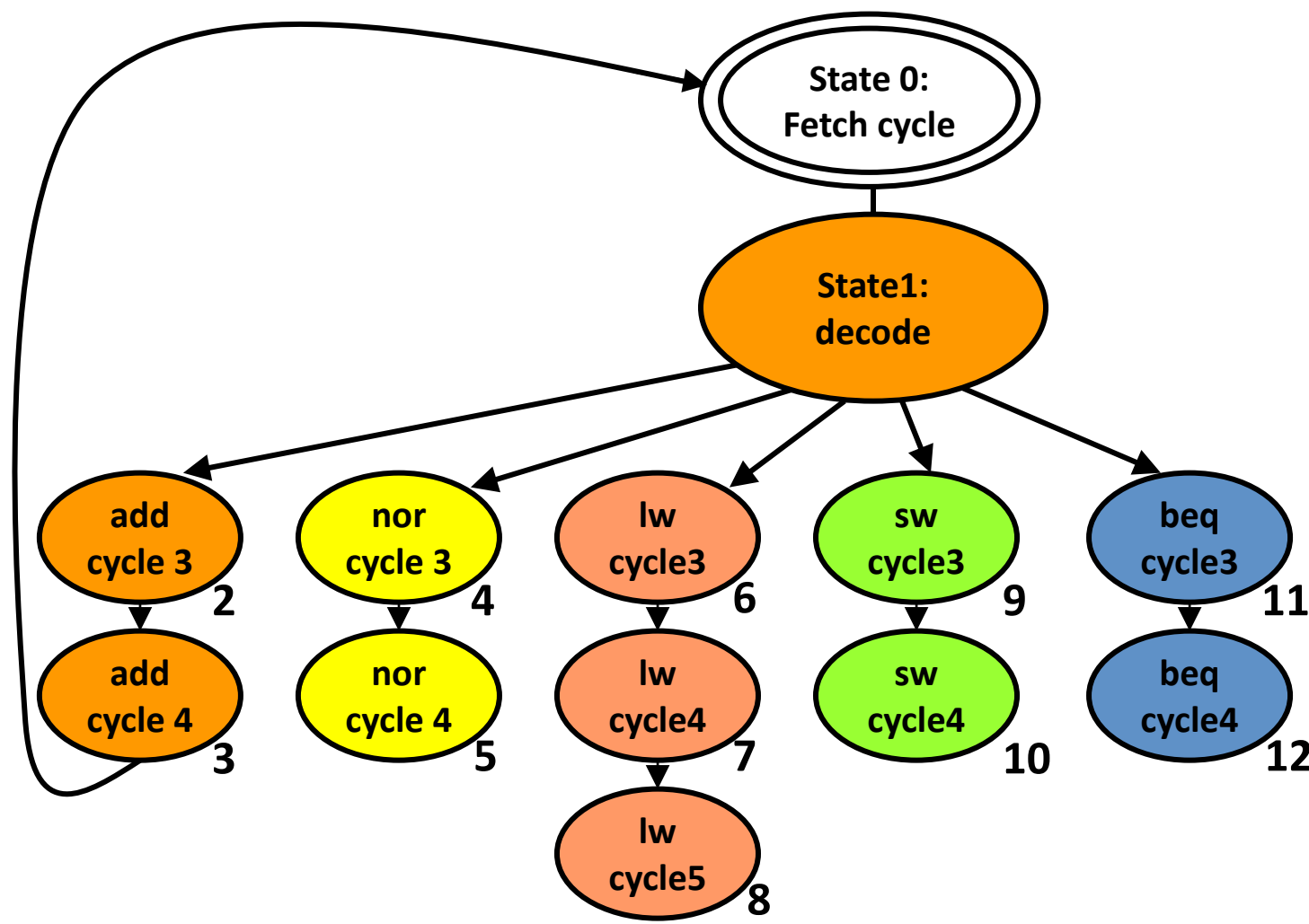


# State 1: Instruction Decode

What will the control bits be?


Update PC; read registers (regA and regB);  
use opcode to determine next state

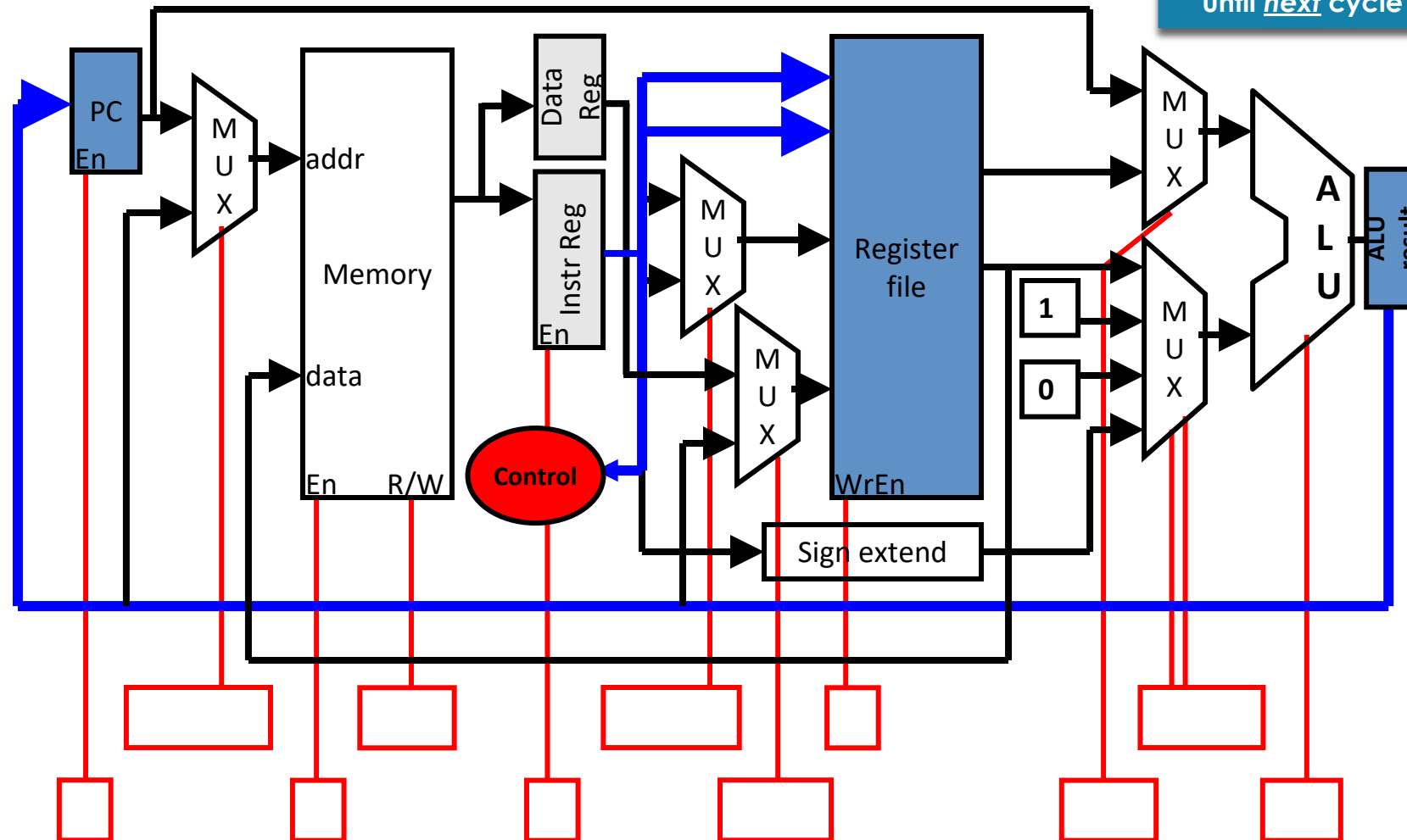Note: since RF read  
latency is same as  
clock period, RF  
data isn't available  
until next cycle




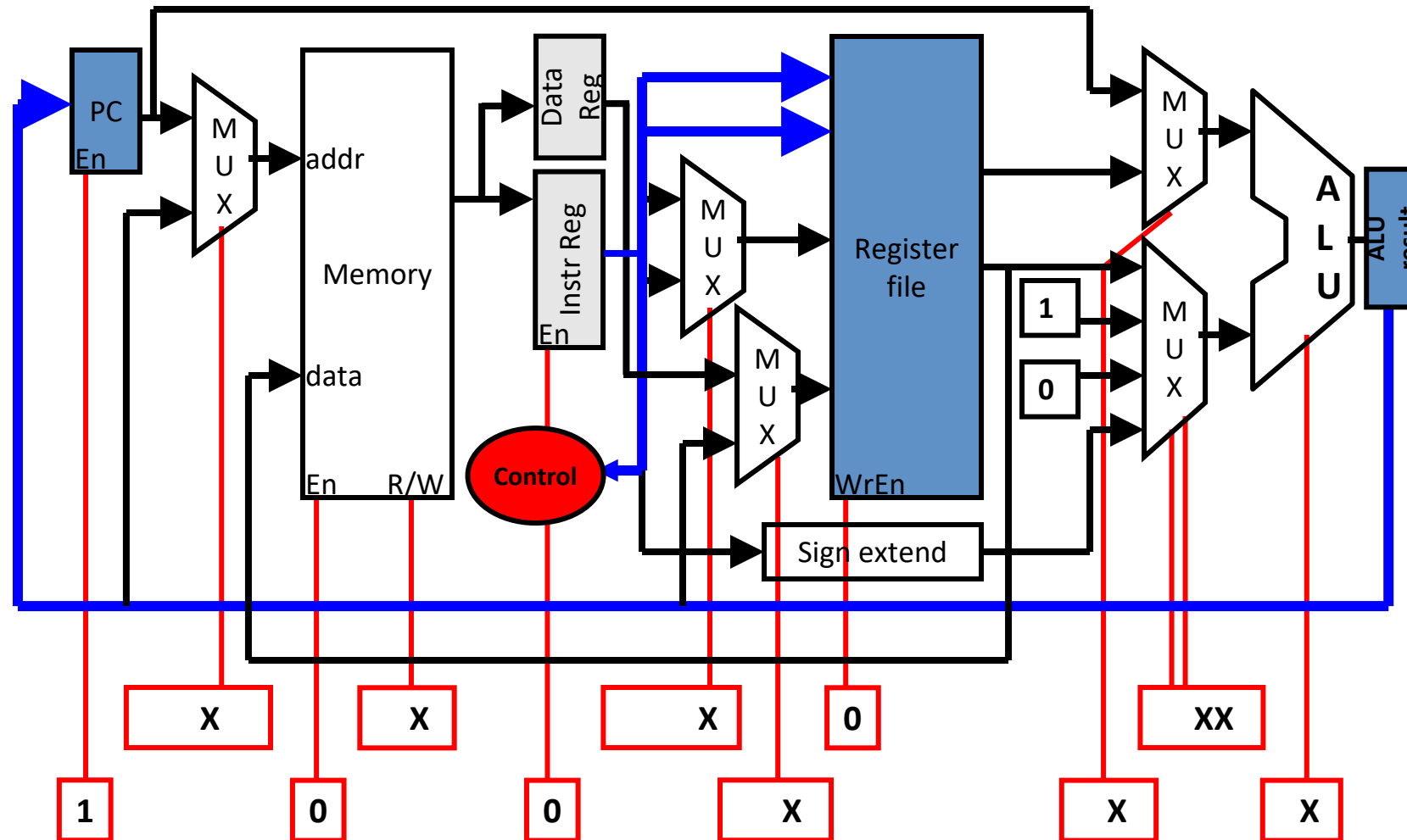
# State 1: output function

Update PC; read registers (regA and regB);  
use opcode to determine next state






# Building the Control Rom

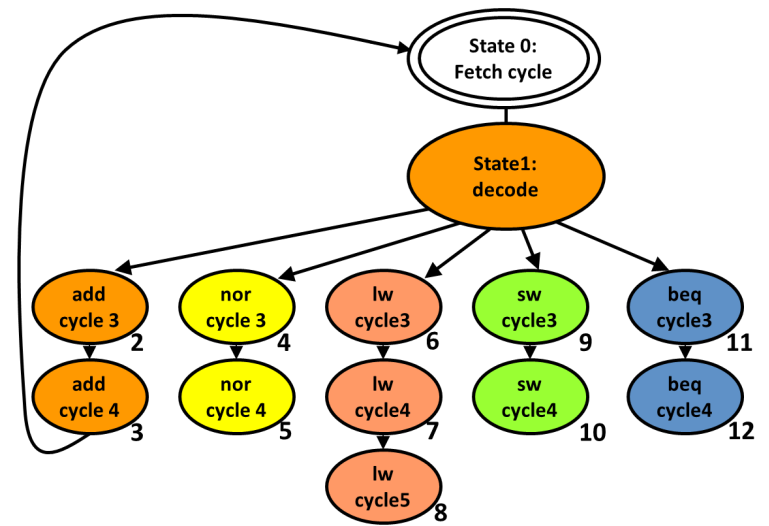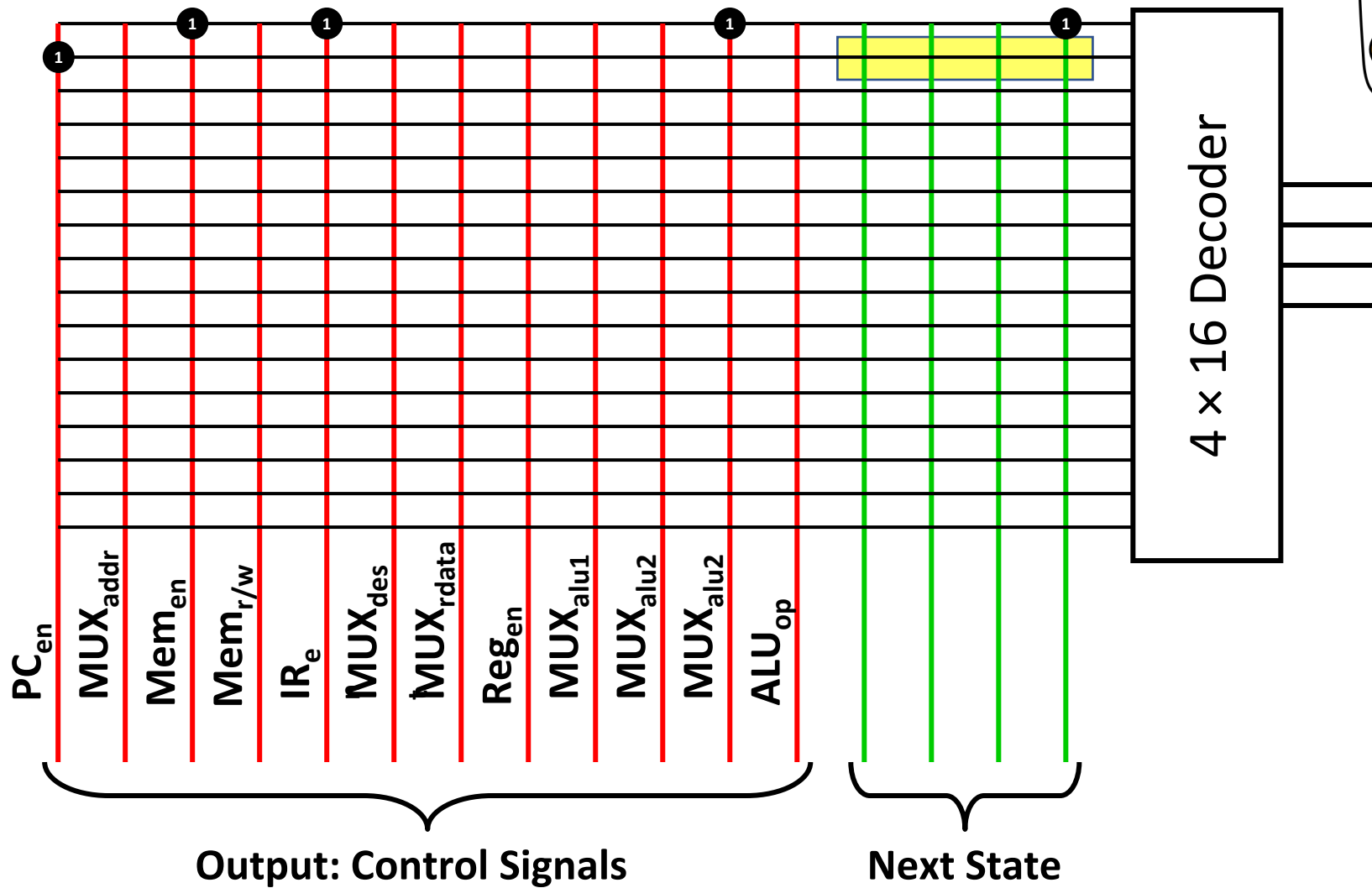


# Transitioning from Decode State

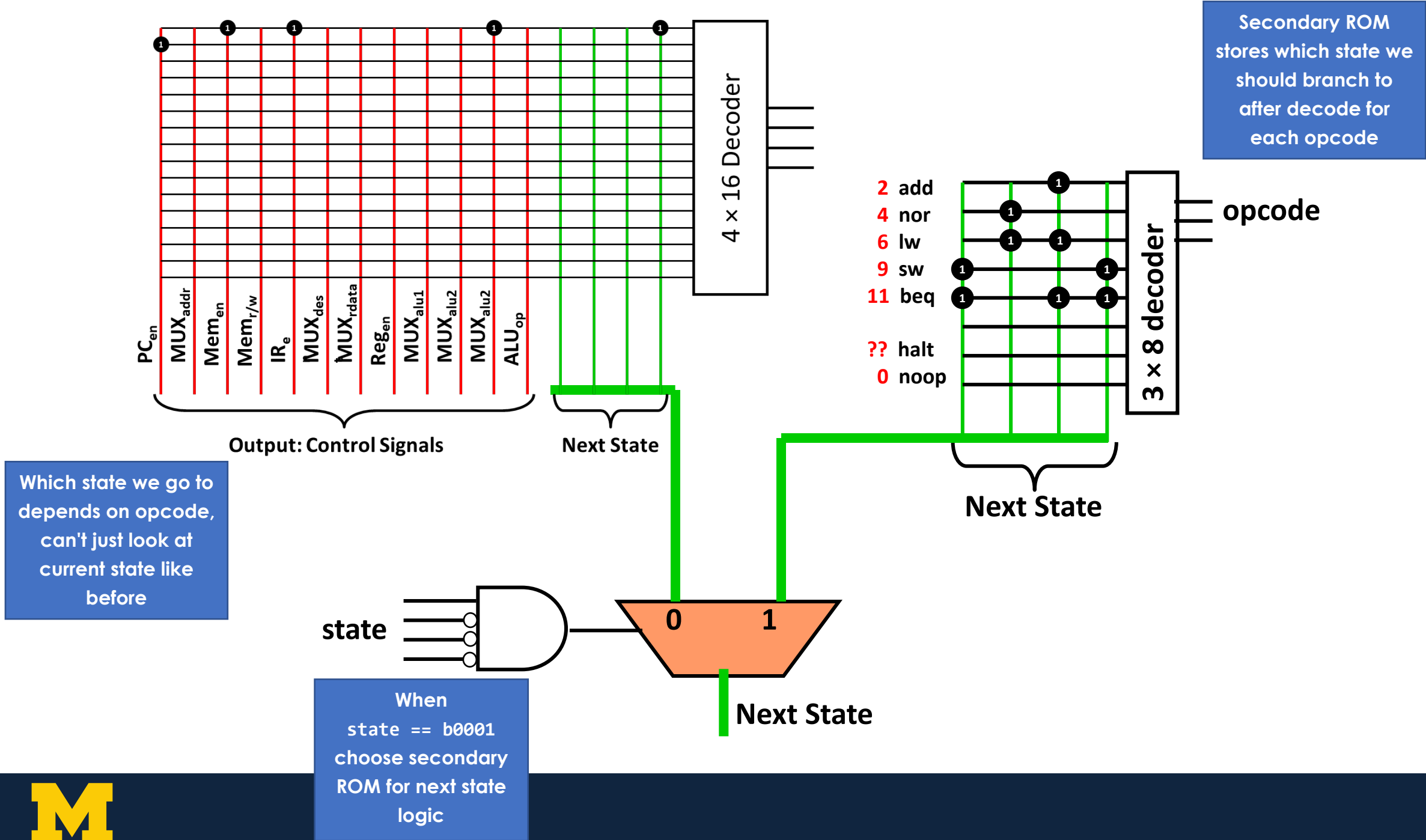

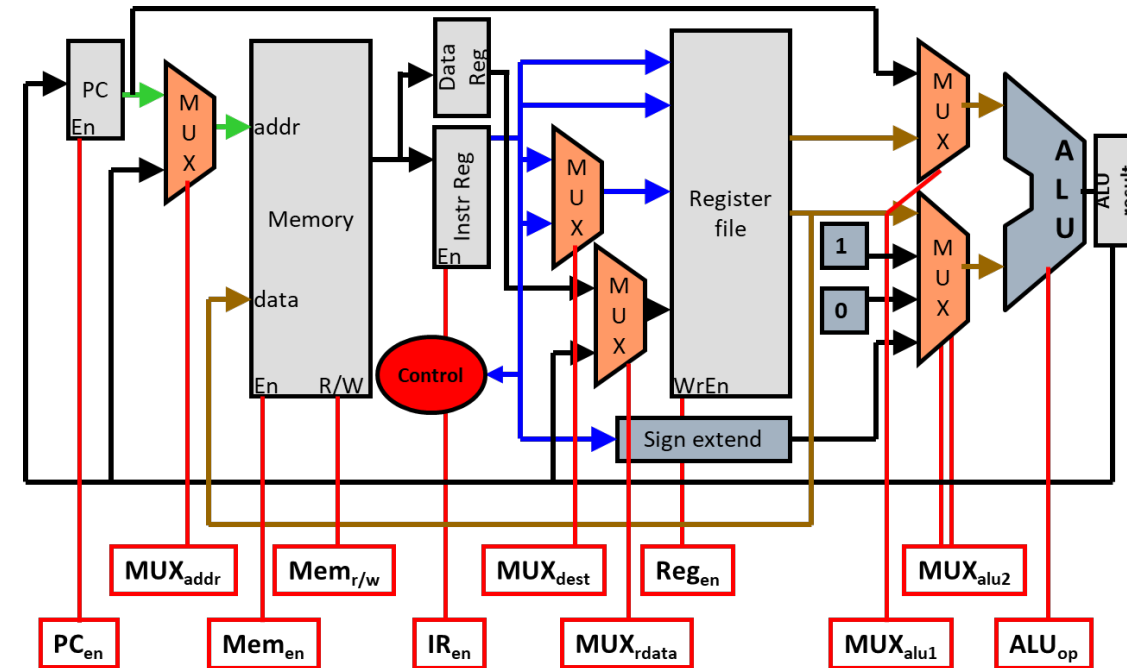
# What do we need to do during Add?

- $\text{Reg}[\text{DestReg}] = \text{Reg}[\text{RegA}] + \text{Reg}[\text{RegB}]$ 
  - Step 1:  $\text{ALU\_Result} \leftarrow \text{Reg}[\text{RegA}] + \text{Reg}[\text{RegB}]$
  - Step 2:  $\text{Reg}[\text{DestReg}] \leftarrow \text{ALU\_Result}$




## State 2: Add cycle 3

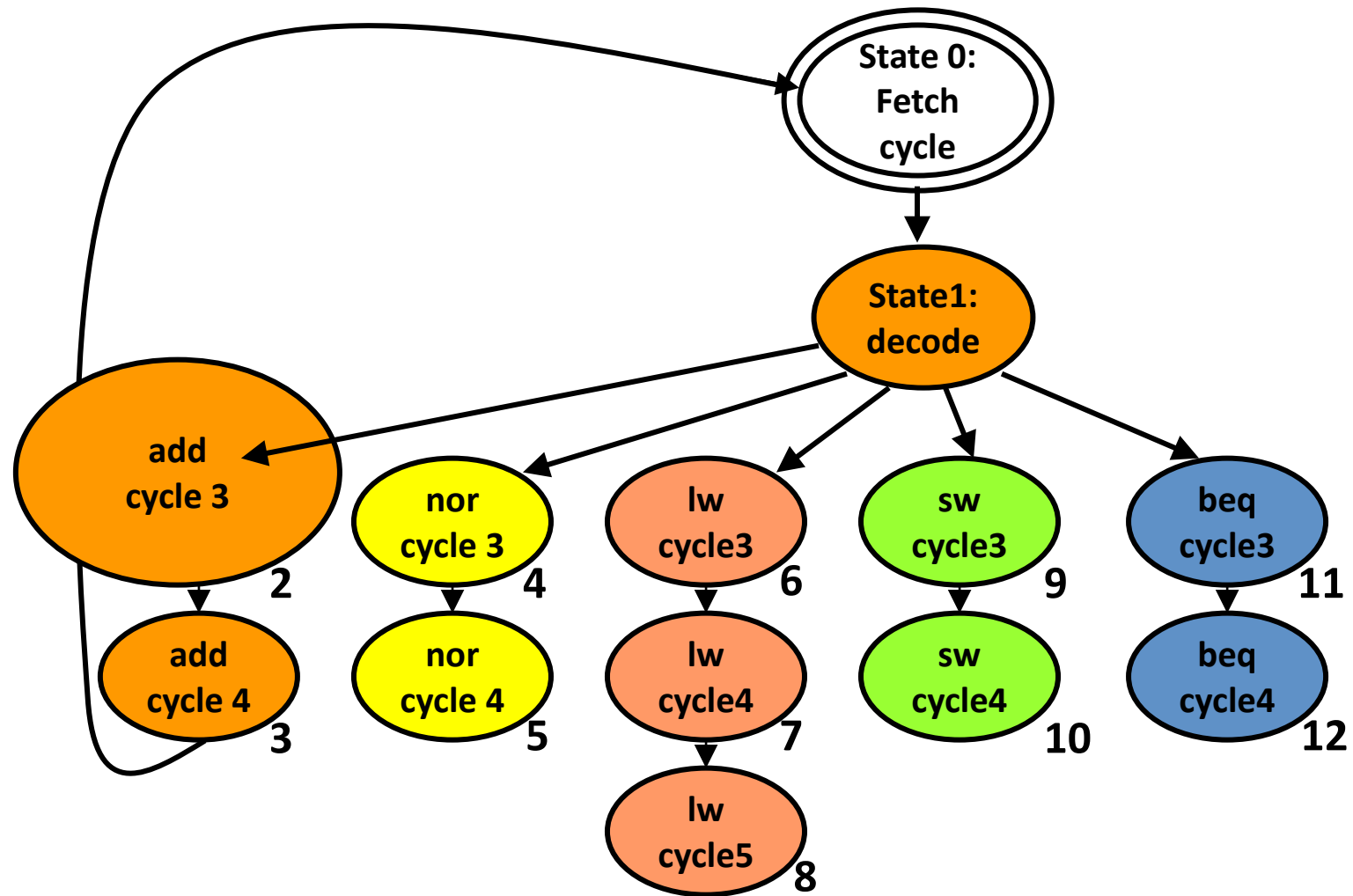

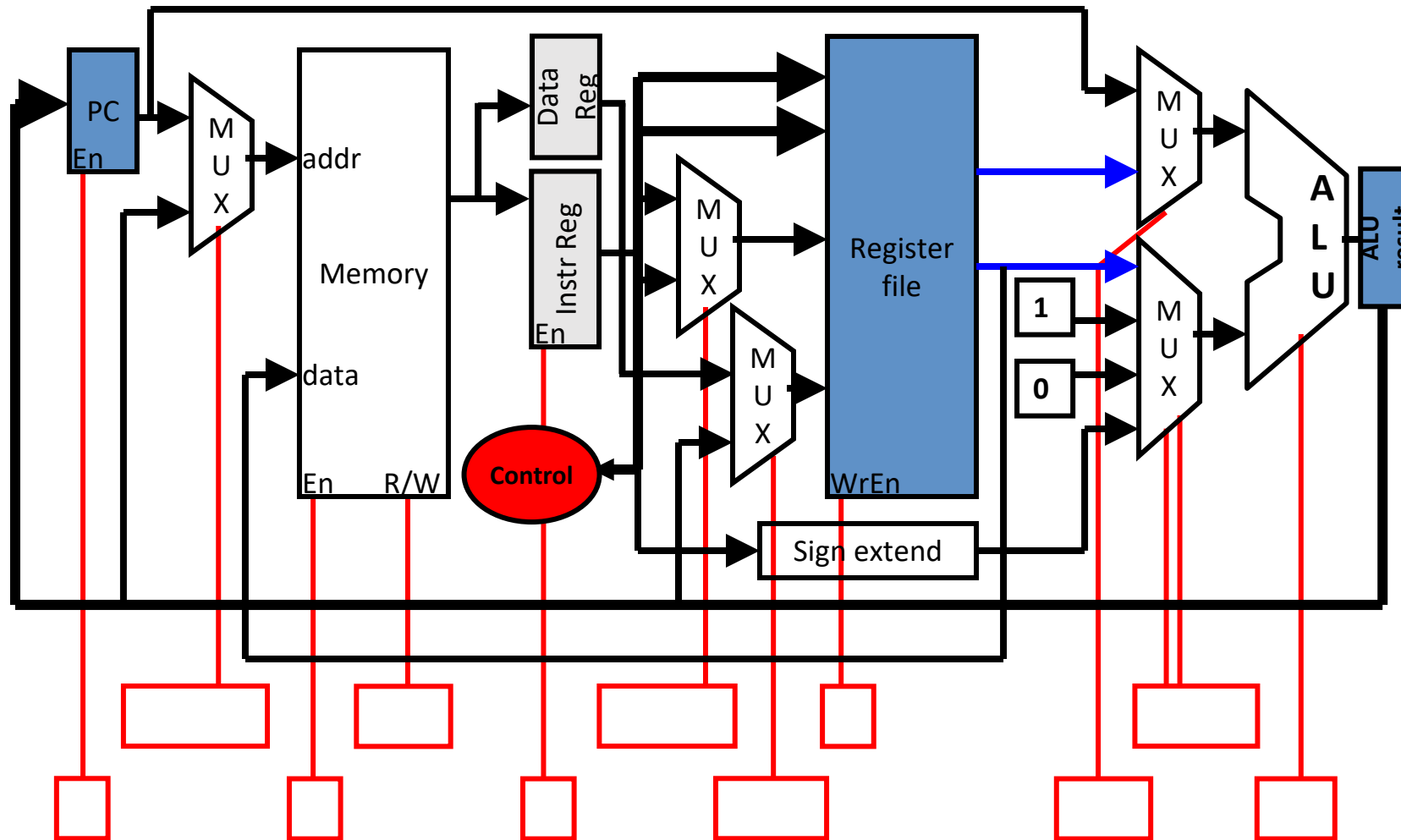
## State 2: **Add** Cycle 3 Operation

$AR \leftarrow \text{Reg}[\text{RegA}] + \text{Reg}[\text{RegB}]$



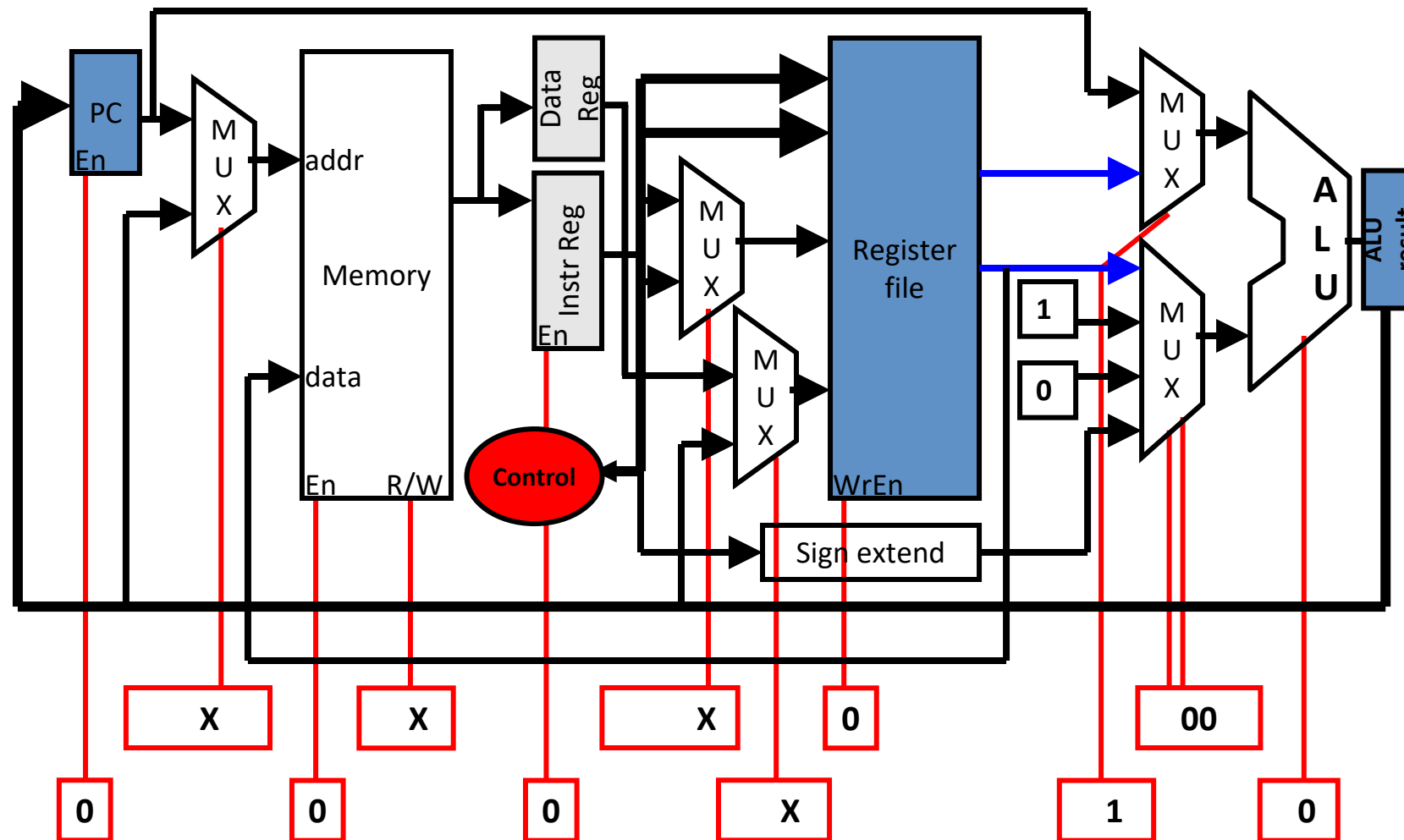
## State 2: **Add** Cycle 3 Operation

$$AR \leftarrow \text{Reg}[\text{RegA}] + \text{Reg}[\text{RegB}]$$




## State 3: Add cycle 4

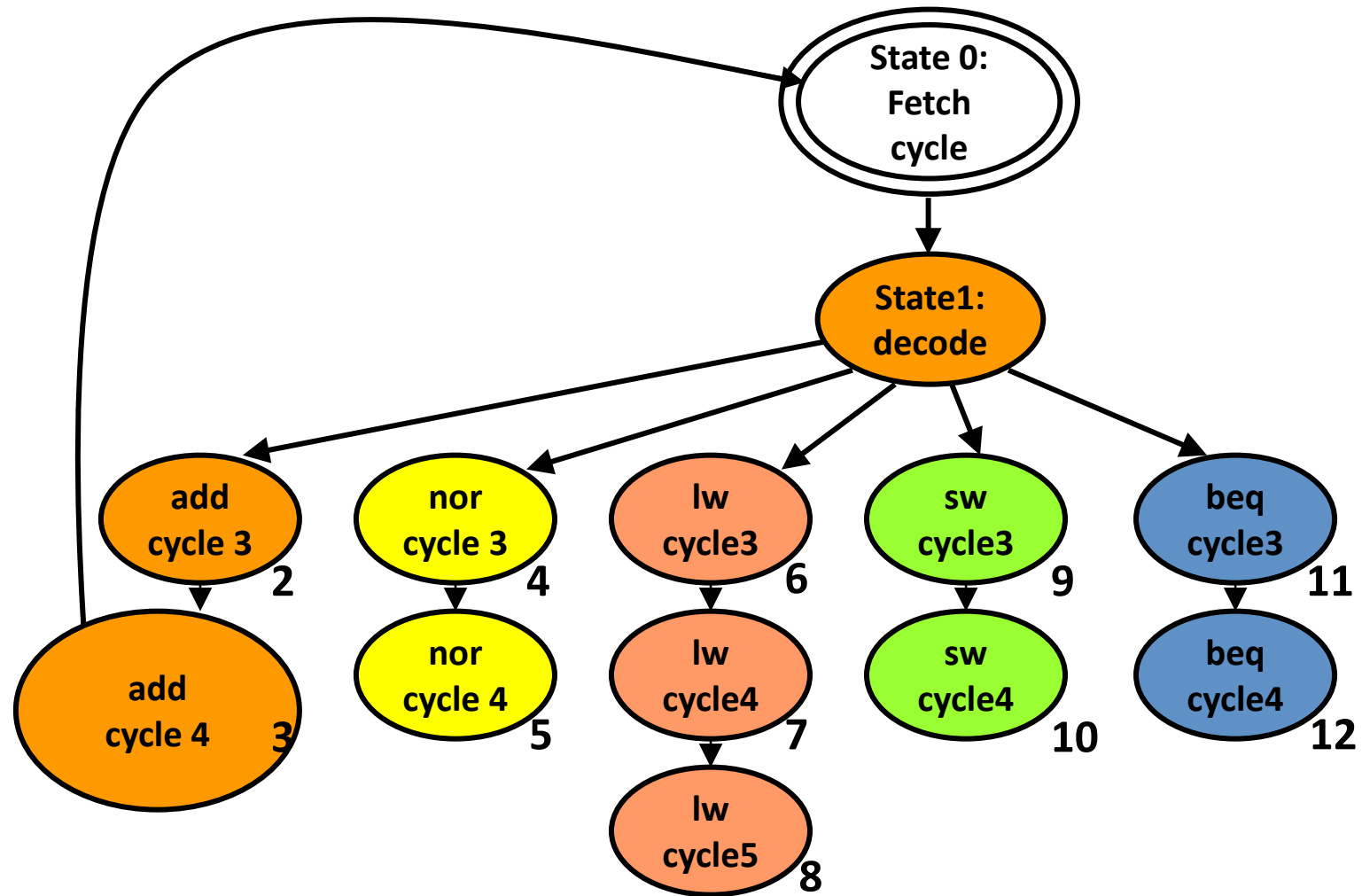
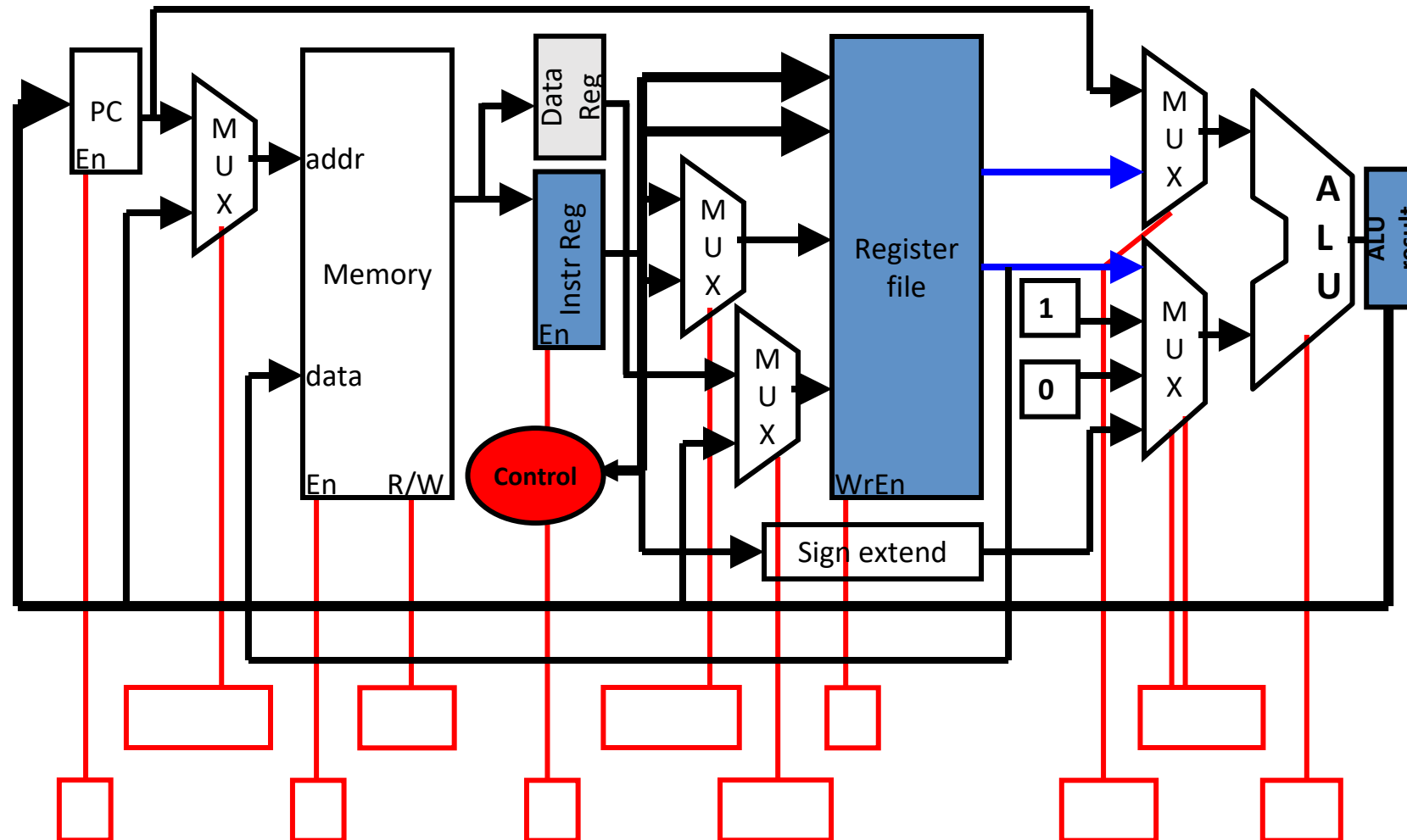
# Add Cycle 4 (State 3) Operation


$\text{Reg}[\text{DestReg}] \leftarrow \text{ALU\_Result}$





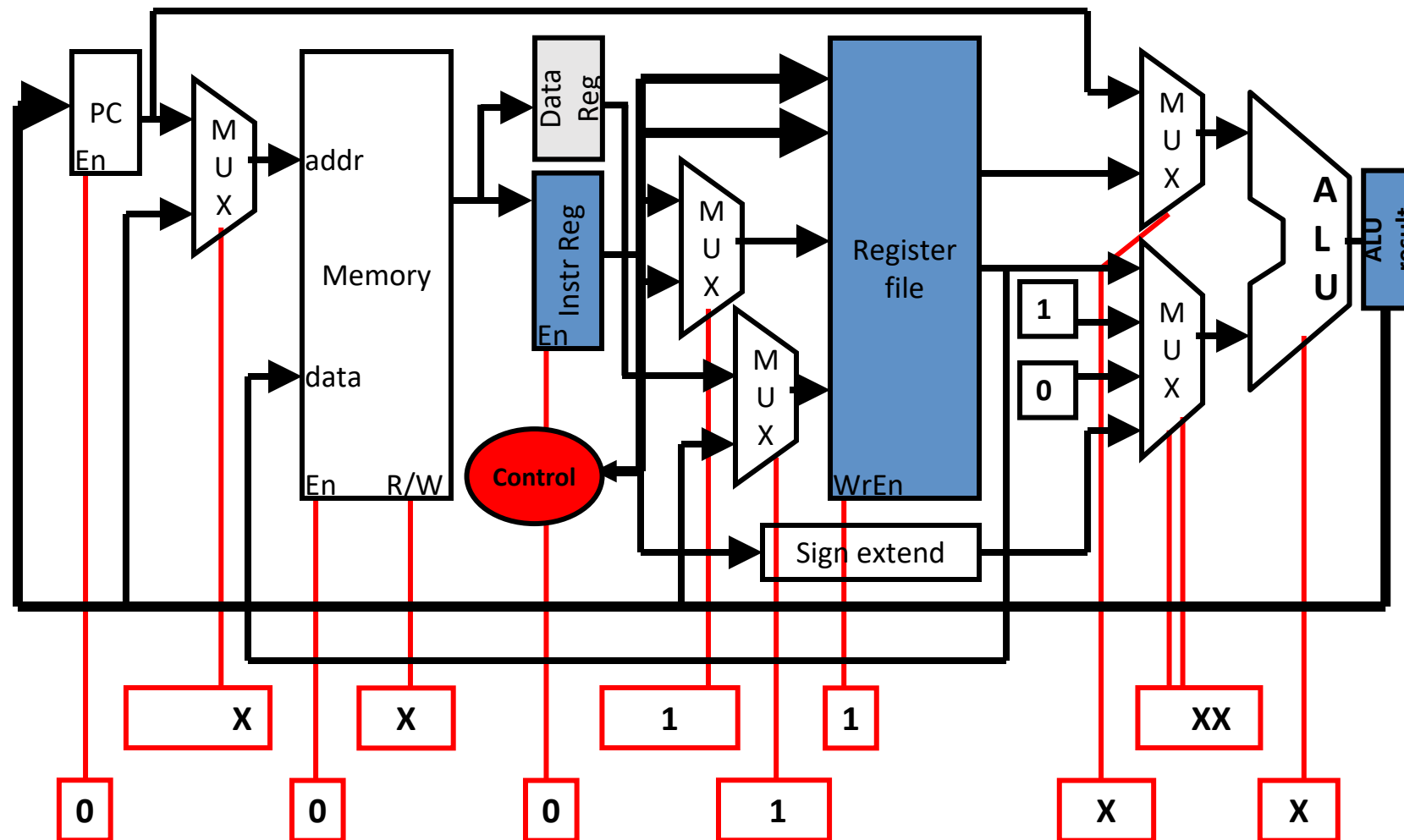
# Add Cycle 4 (State 3) Operation


$\text{Reg}[\text{DestReg}] \leftarrow \text{ALU\_Result}$




# Building the Control Rom

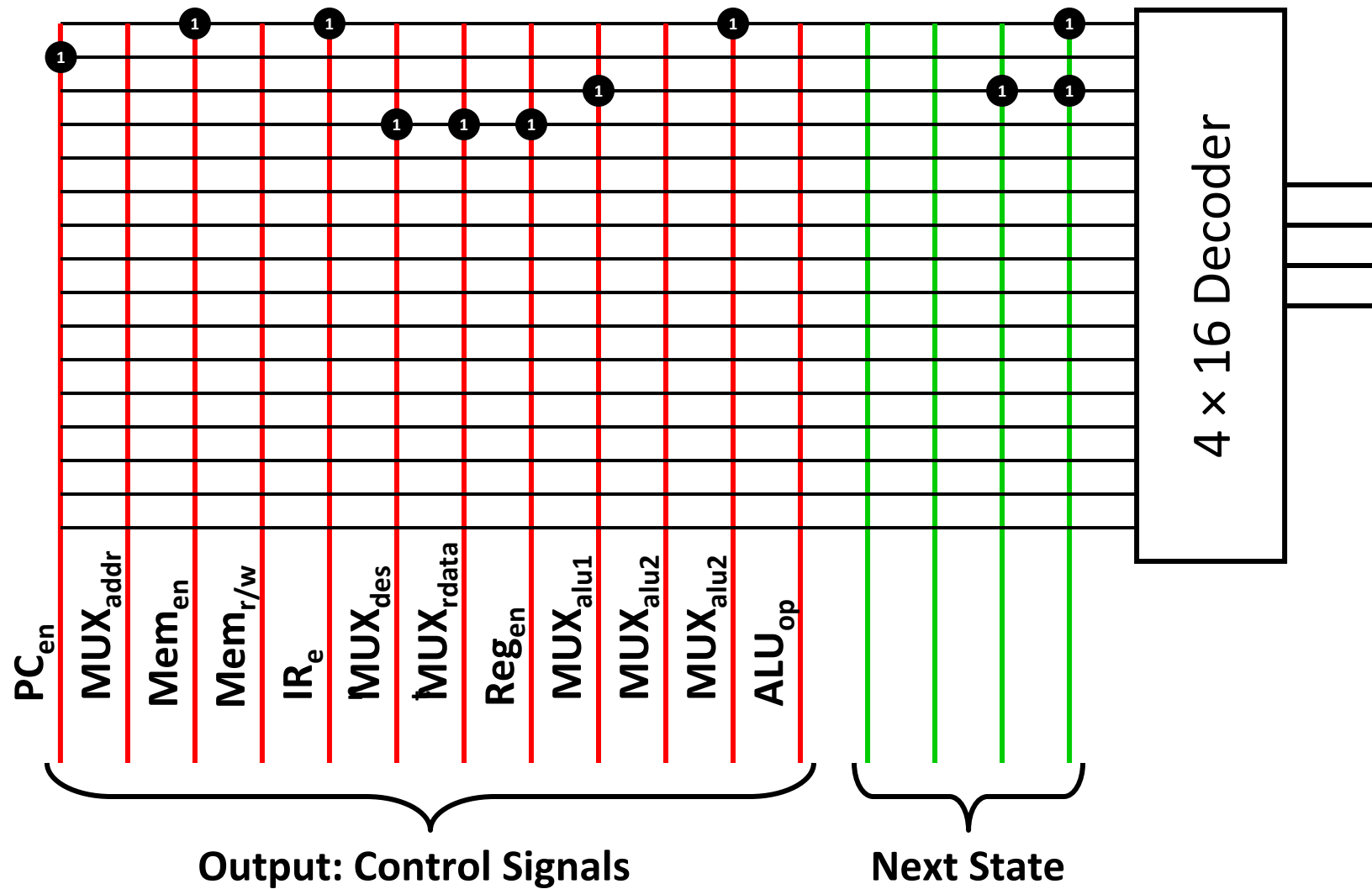
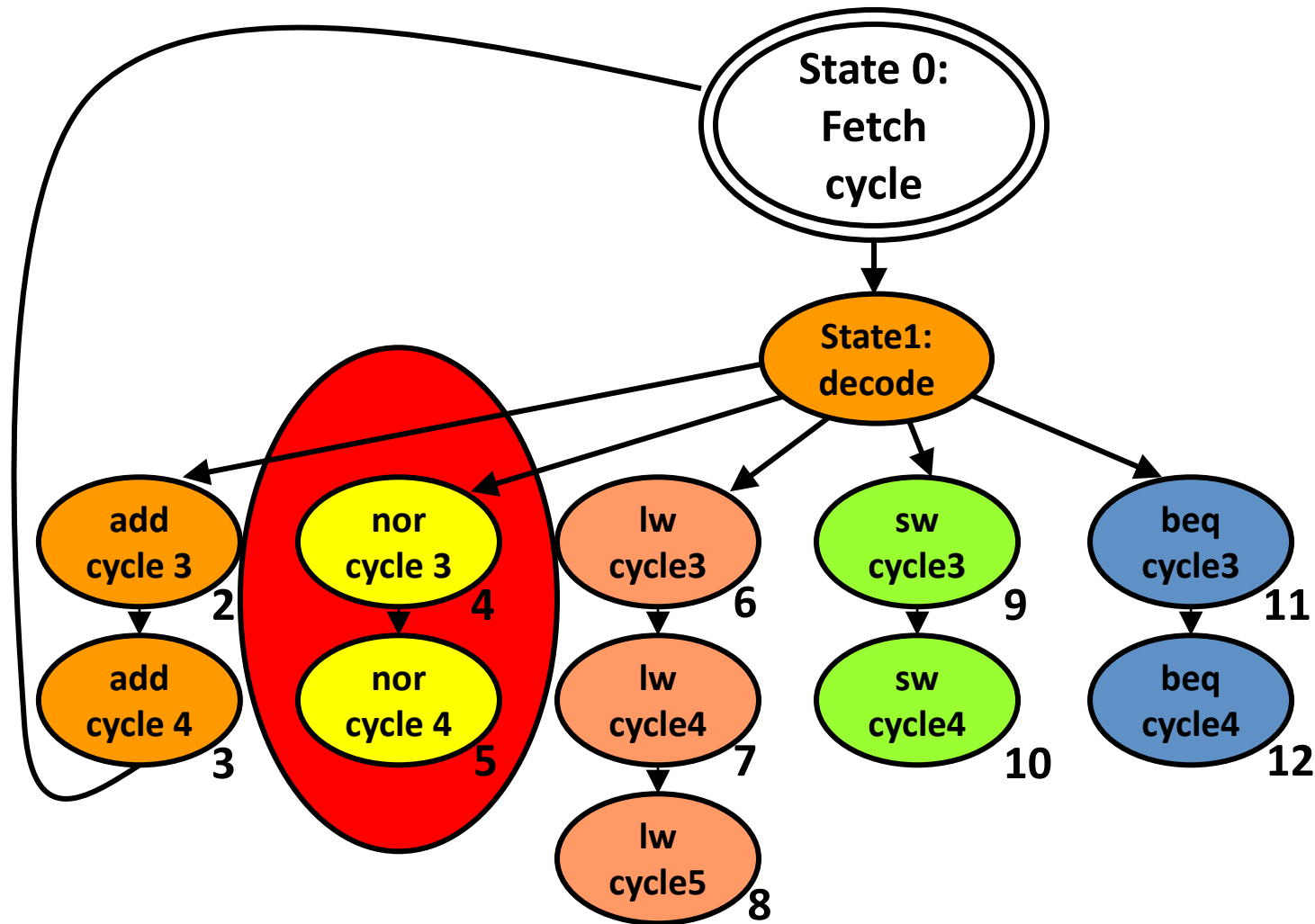
# Return to State 0: Fetch cycle to execute the next instruction




## Control Rom for nor (4 and 5)

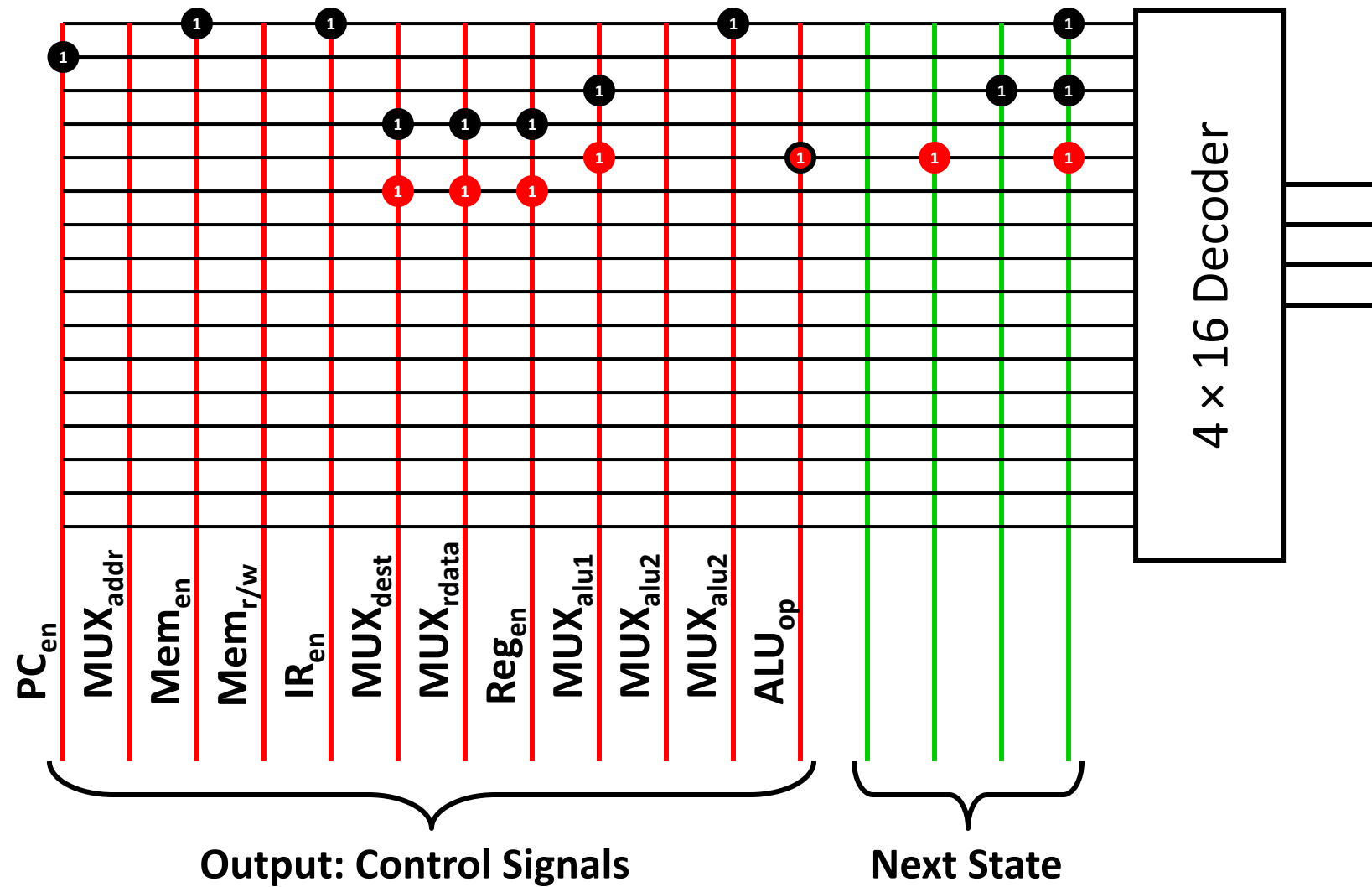

Same output as  
add except  
 $ALU_{op}$  and Next  
State
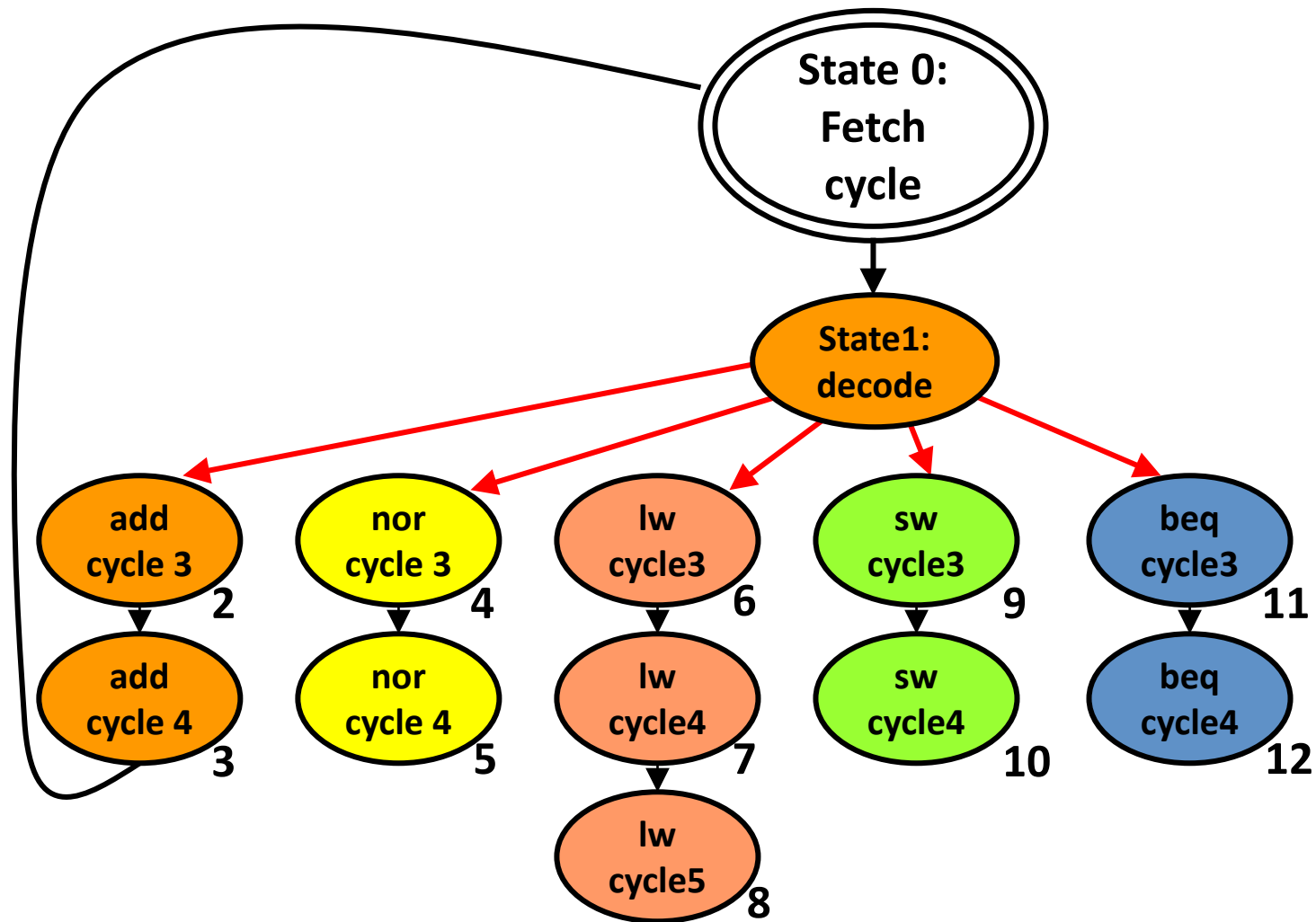
# Return to State 0: Fetch cycle to execute the next instruction




# What do we need to do during LW?




# State 6: LW cycle 3

Calculate address for memory reference

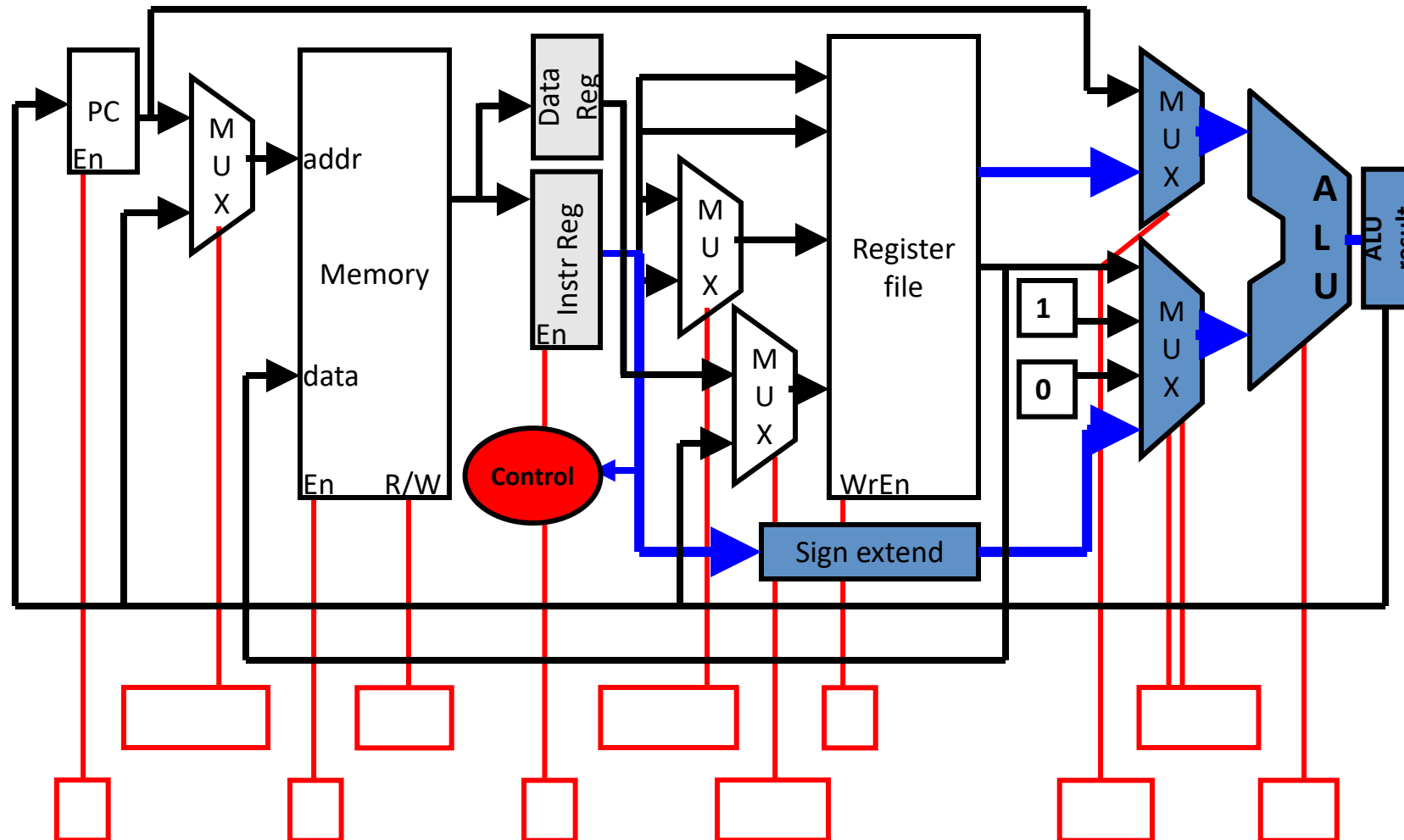


# State 6: LW cycle 3

Calculate address for memory reference

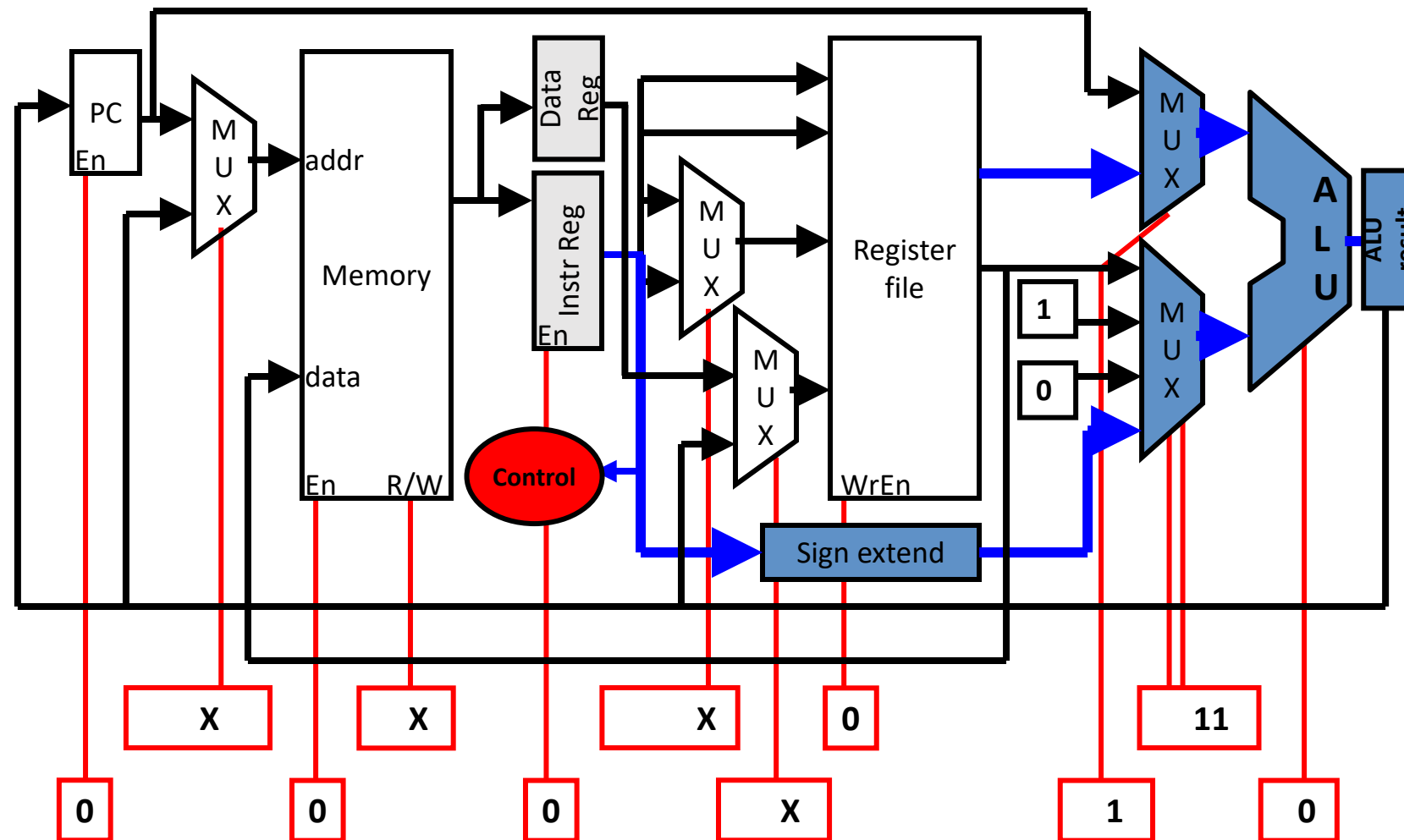




# Control Rom (lw cycle 3)

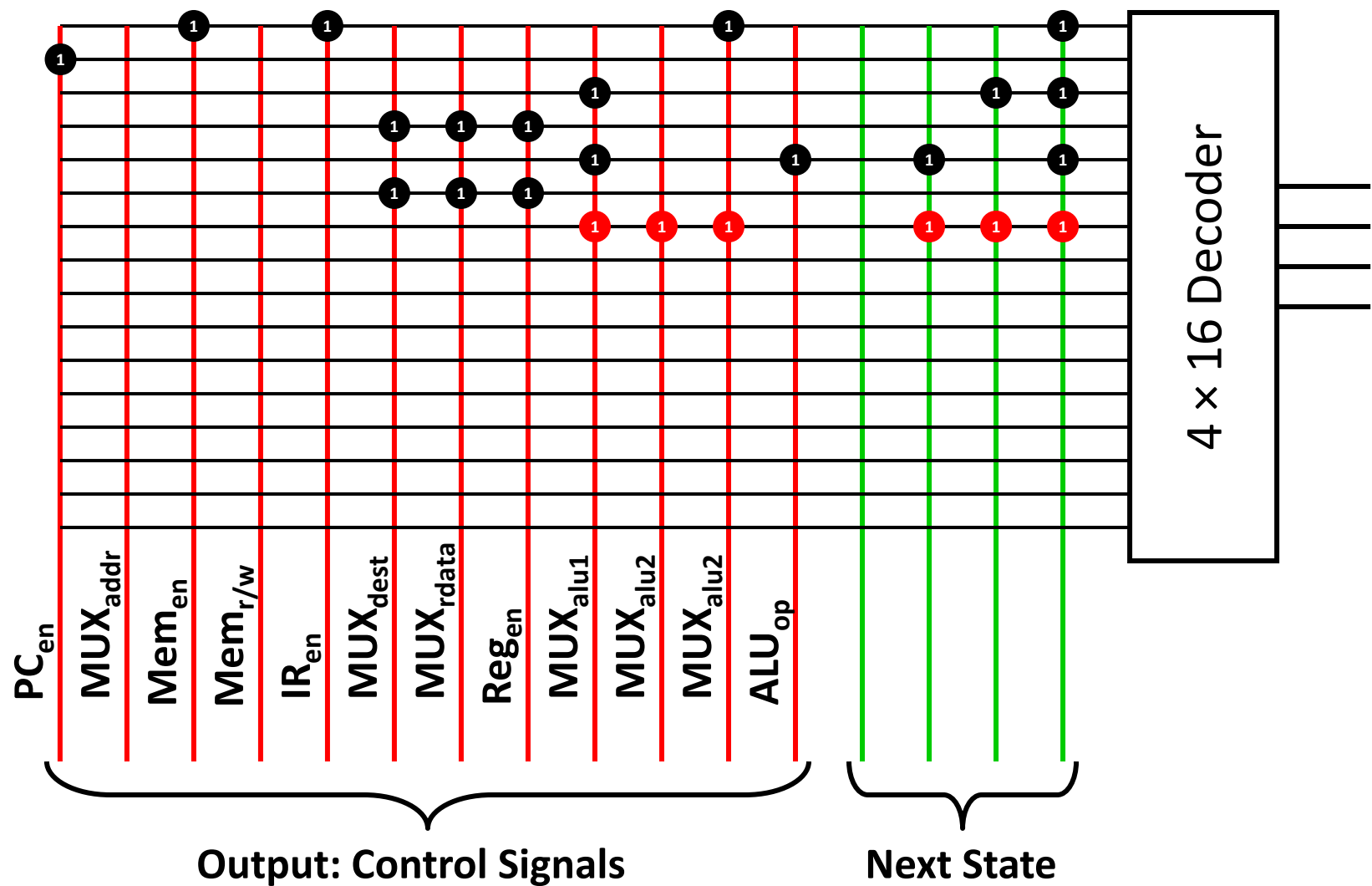


# State 7: LW cycle 4
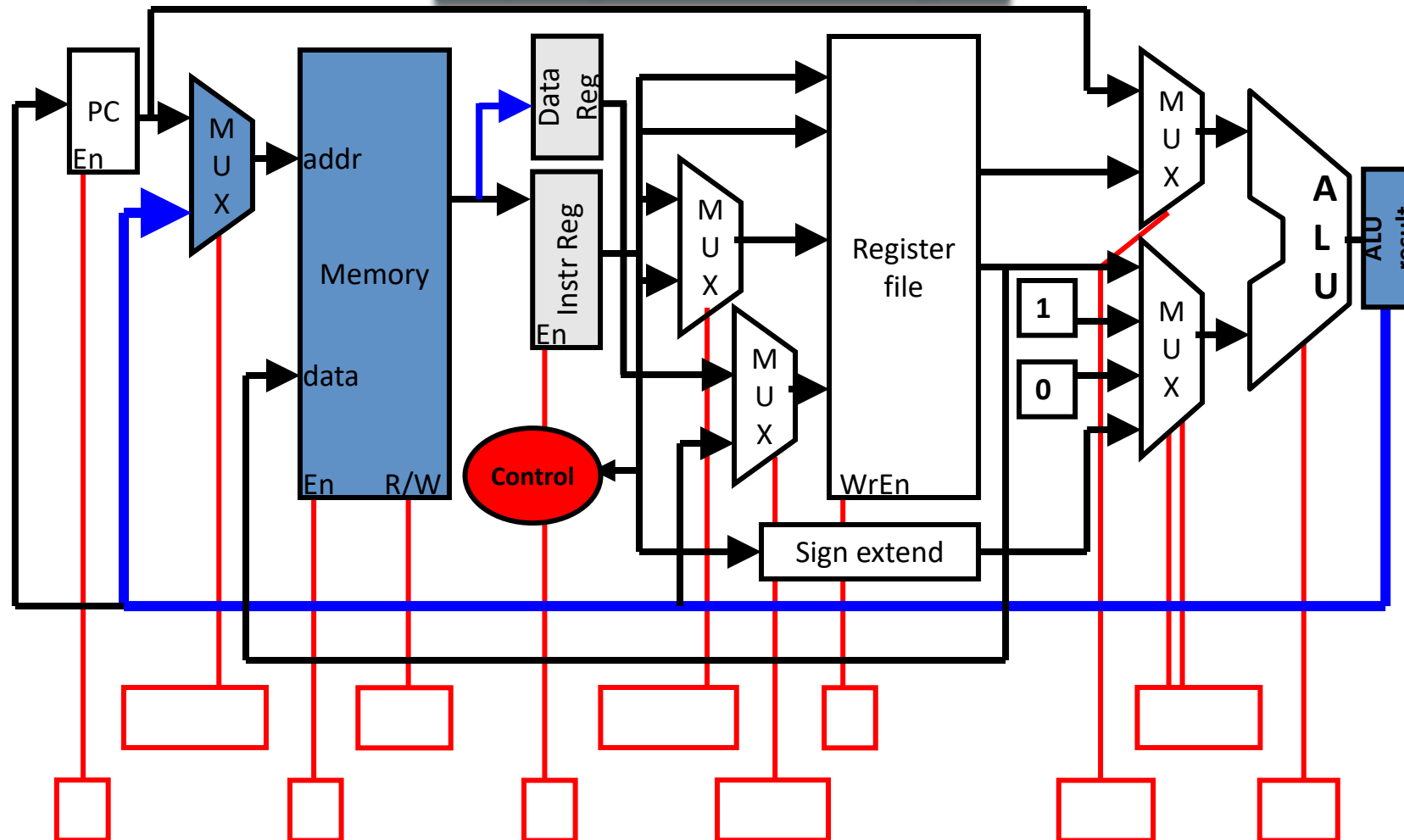
## Read memory location


Loaded data stored in "data" reg  
(analogous to the Instruction Reg)



# State 7: LW cycle 4

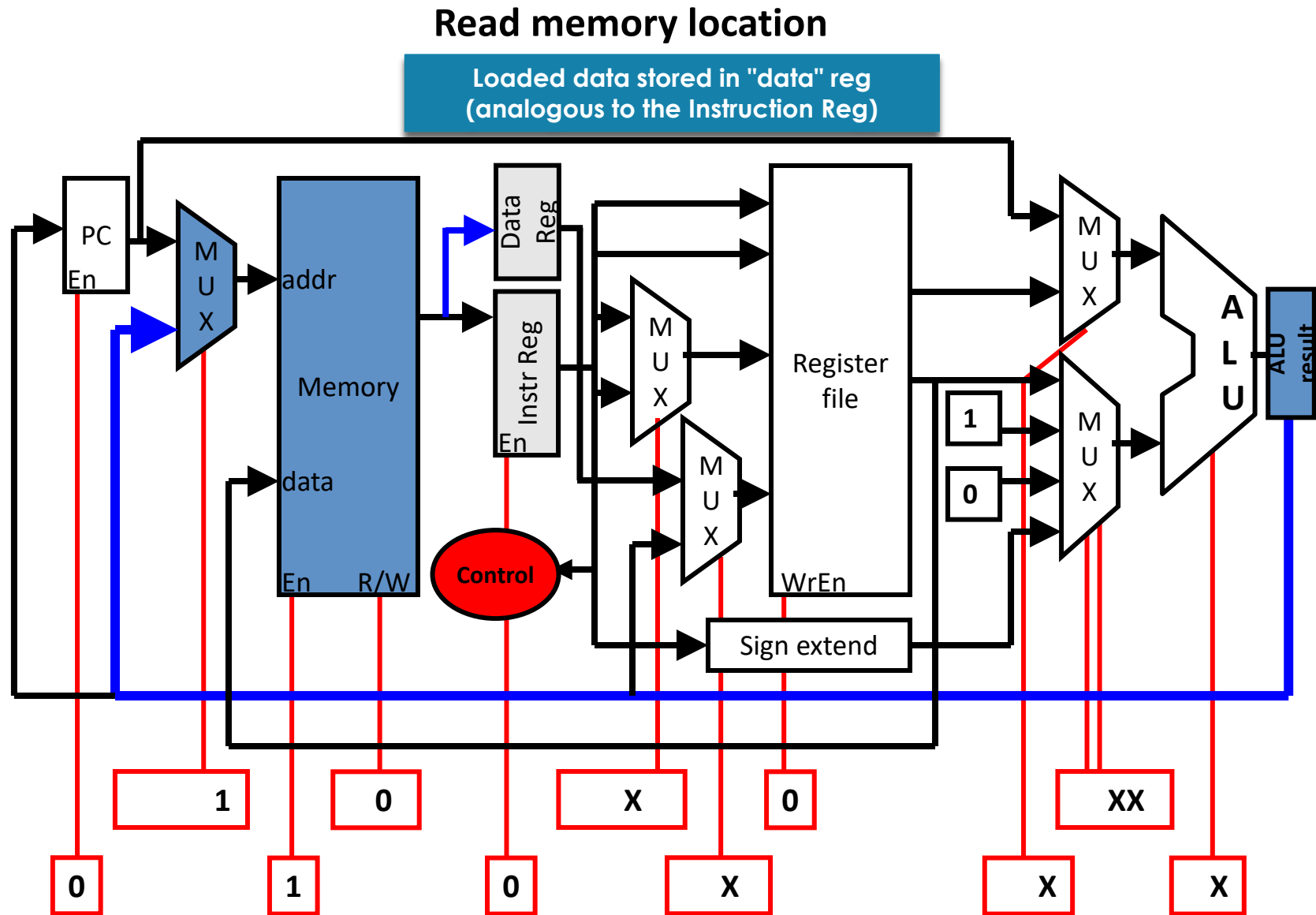


Control Rom (lw cycle 4)

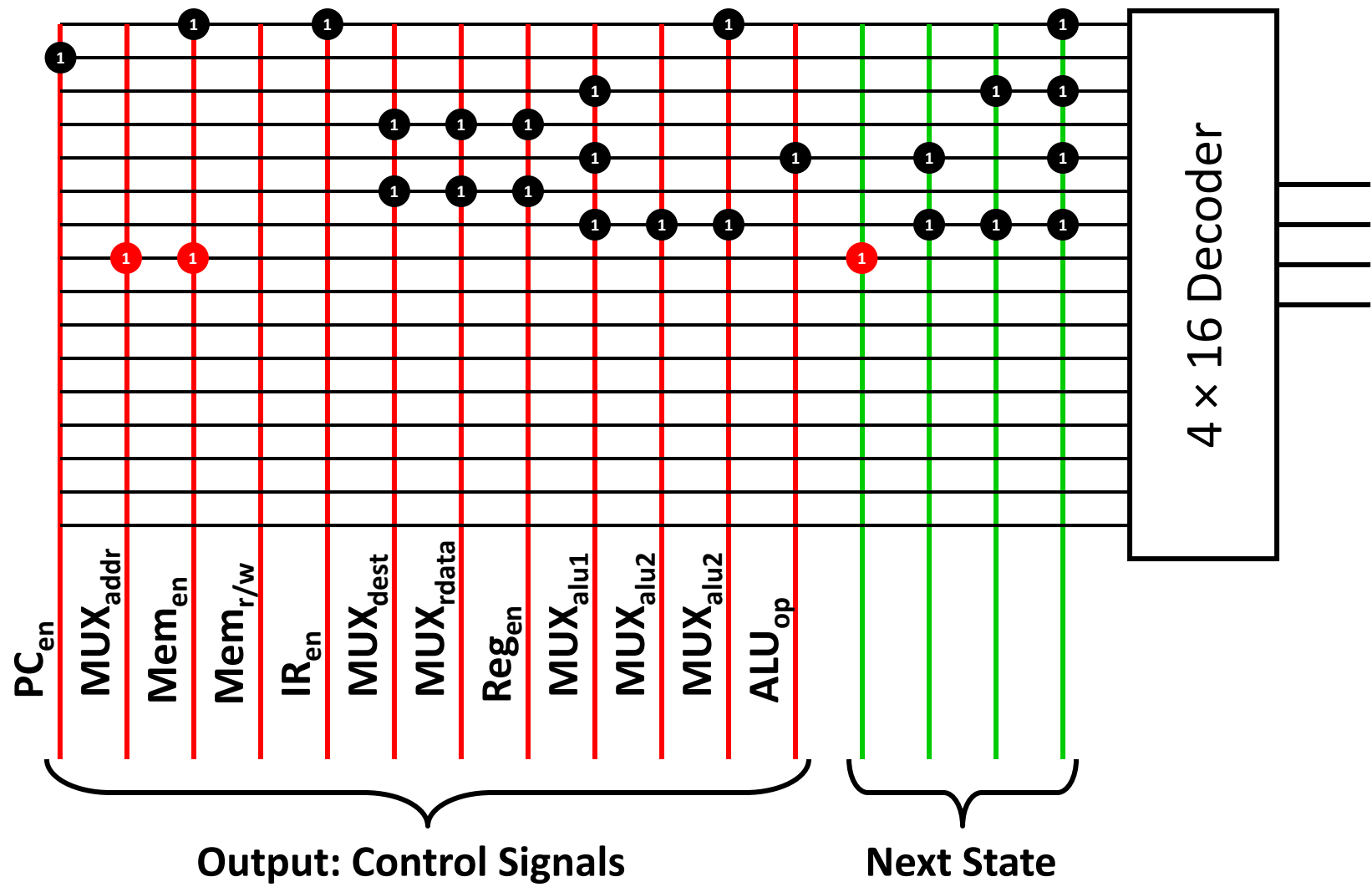


# State 8: LW cycle 5

Write memory value to register file

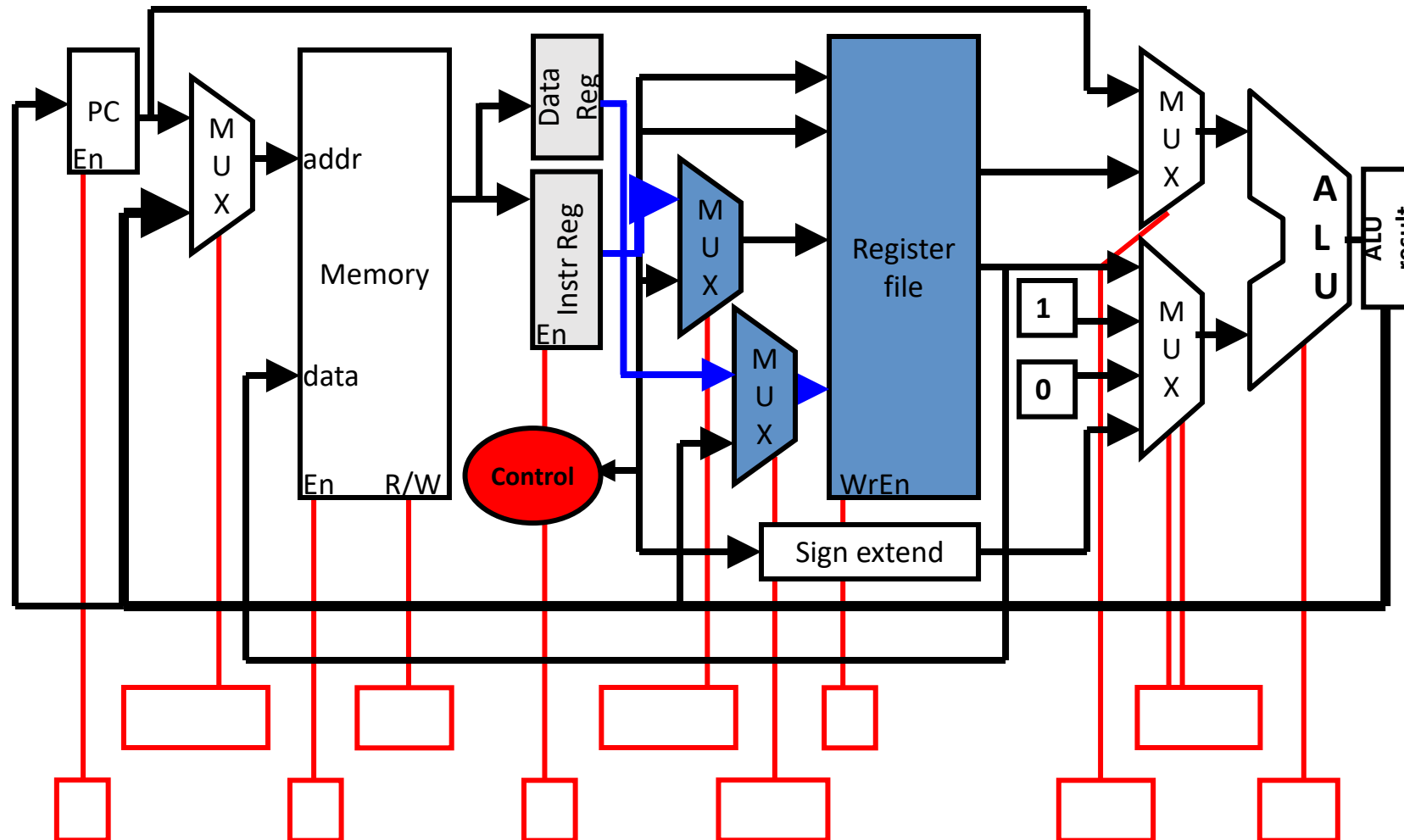


# State 8: LW cycle 5


Write memory value to register file

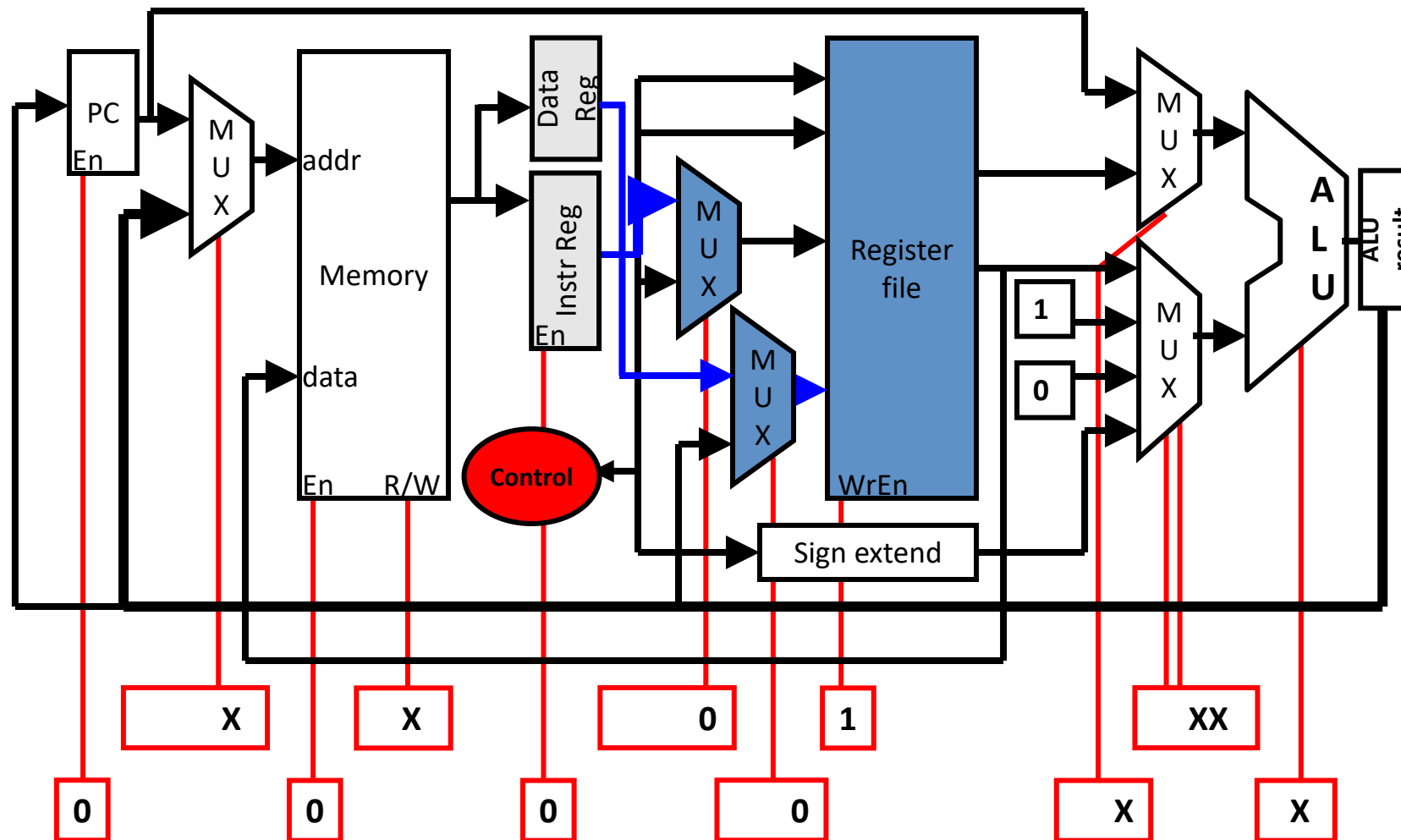

Control Rom (lw cycle 5)

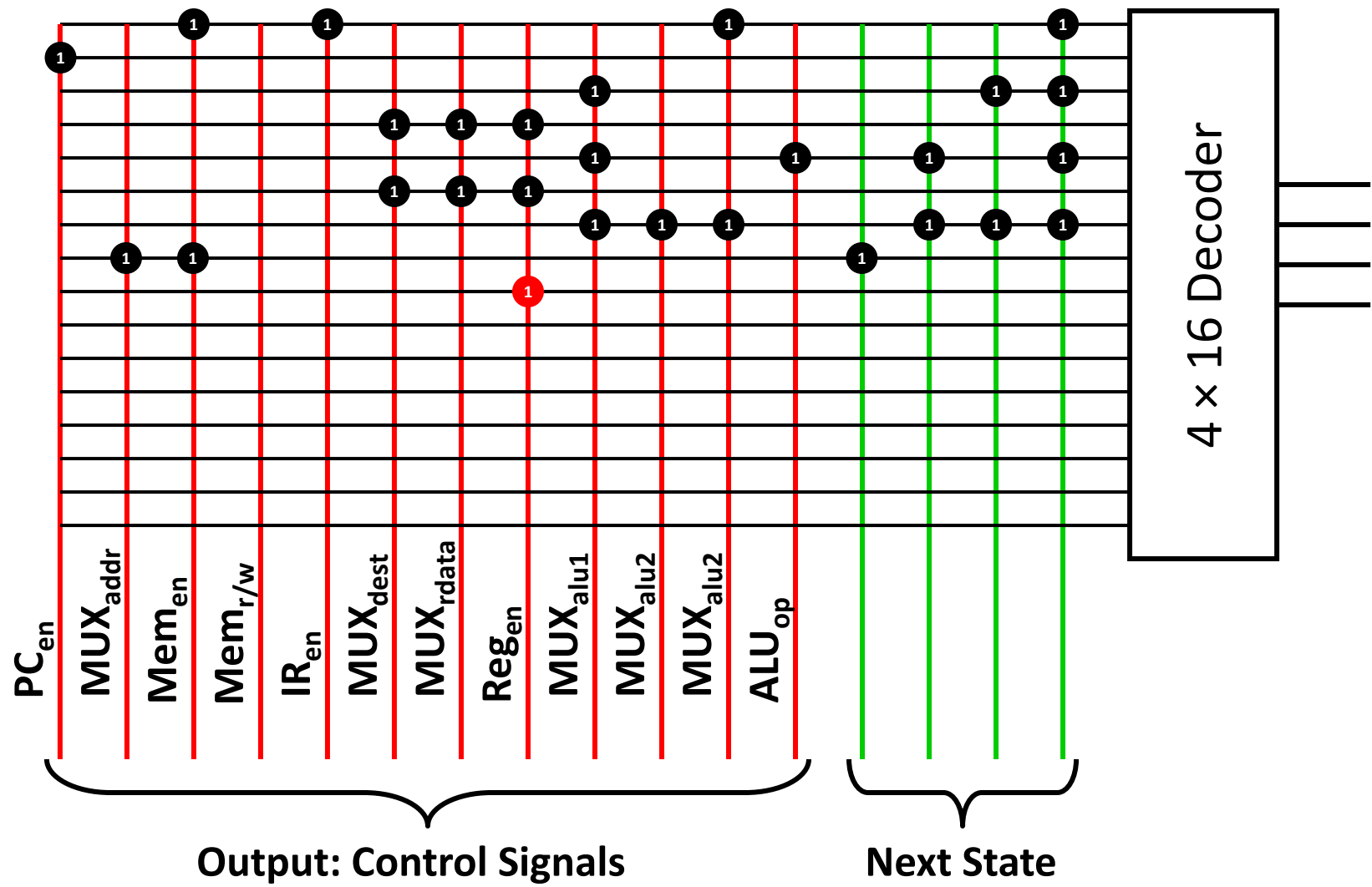
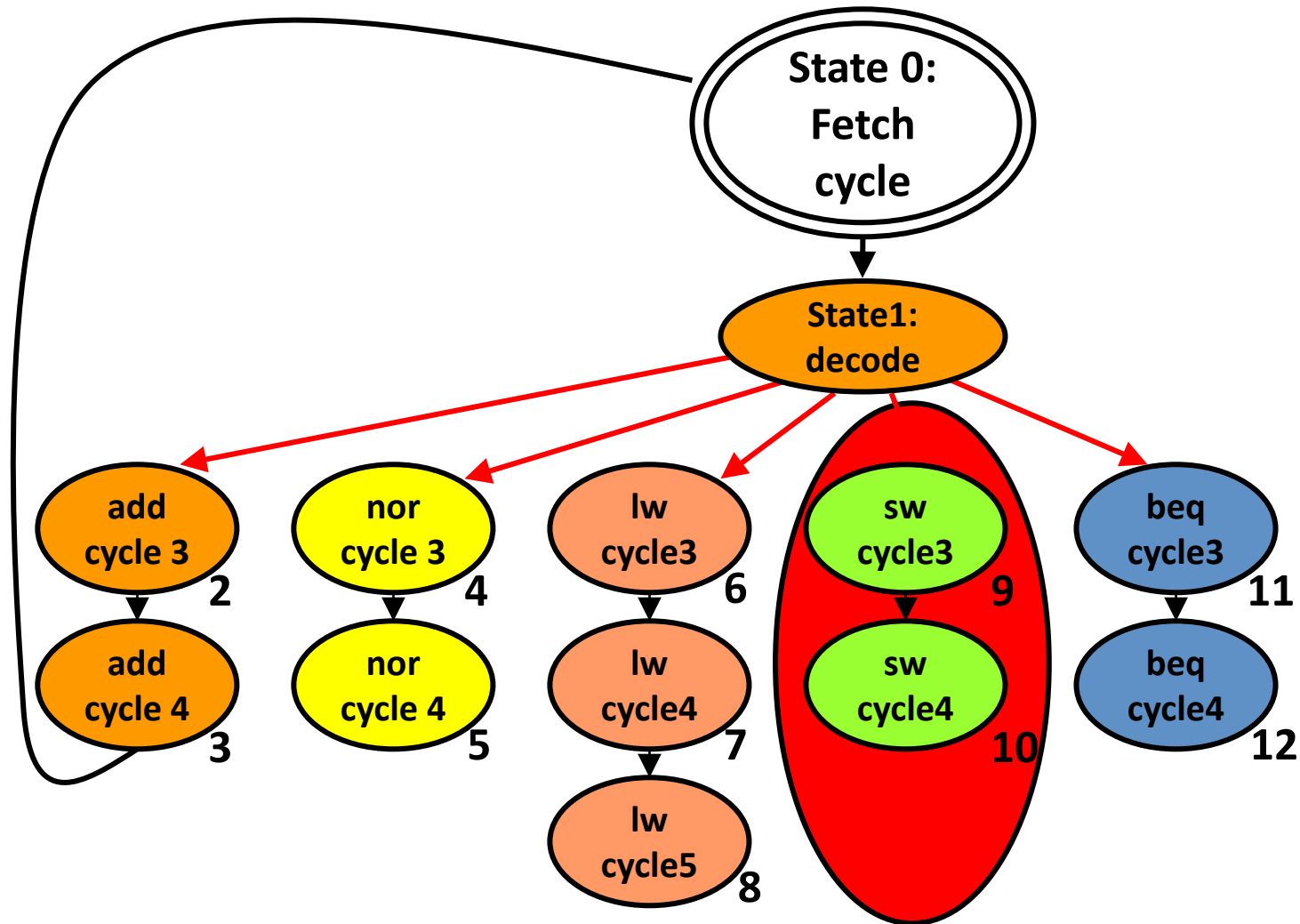
# Return to State 0: Fetch cycle to execute the next instruction






# What do we need to do during SW?




Same as lw, except  $\text{Mem}_{r/w}$  and Next State

## Control Rom (sw cycles 3 and 4)

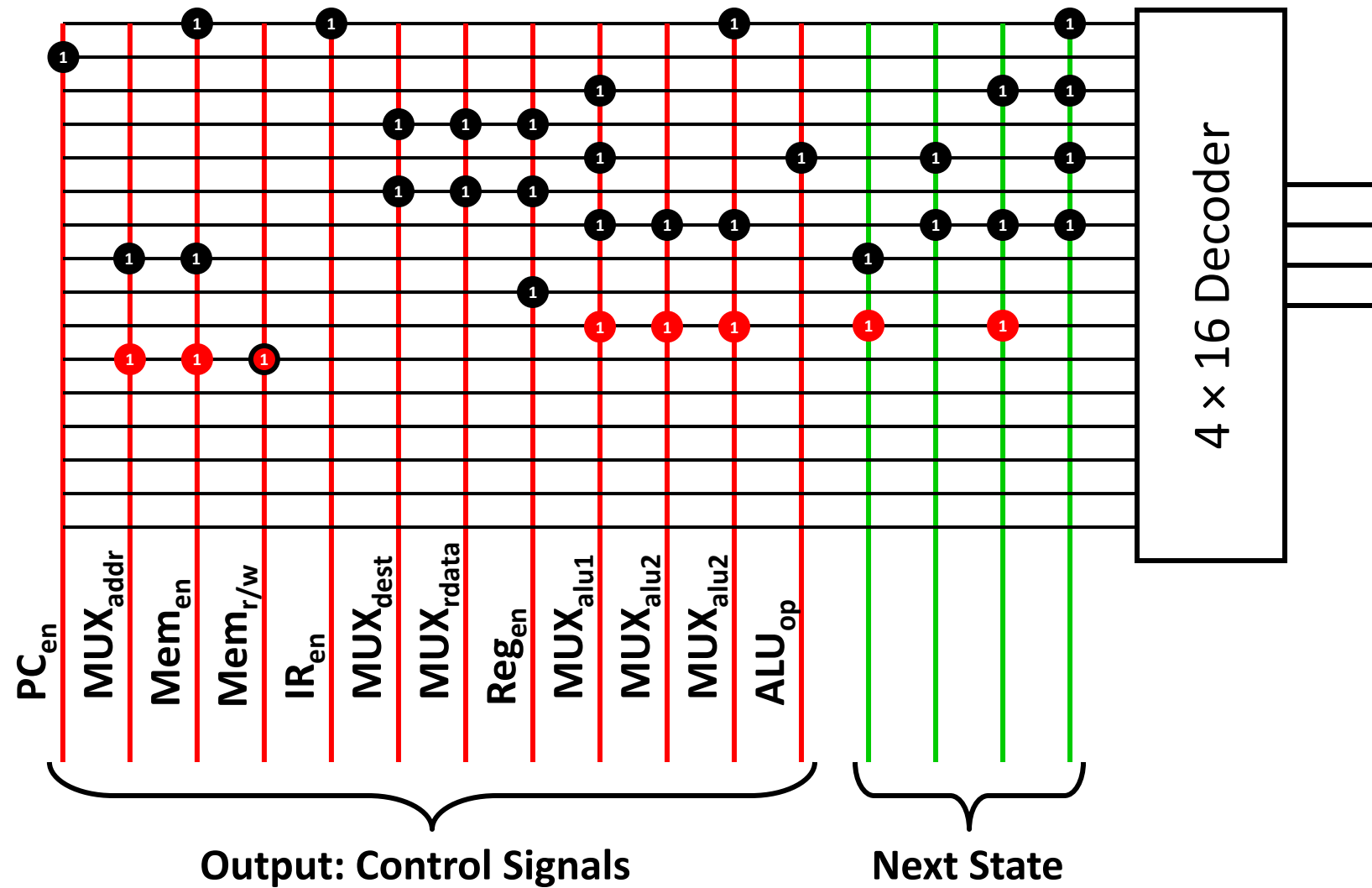
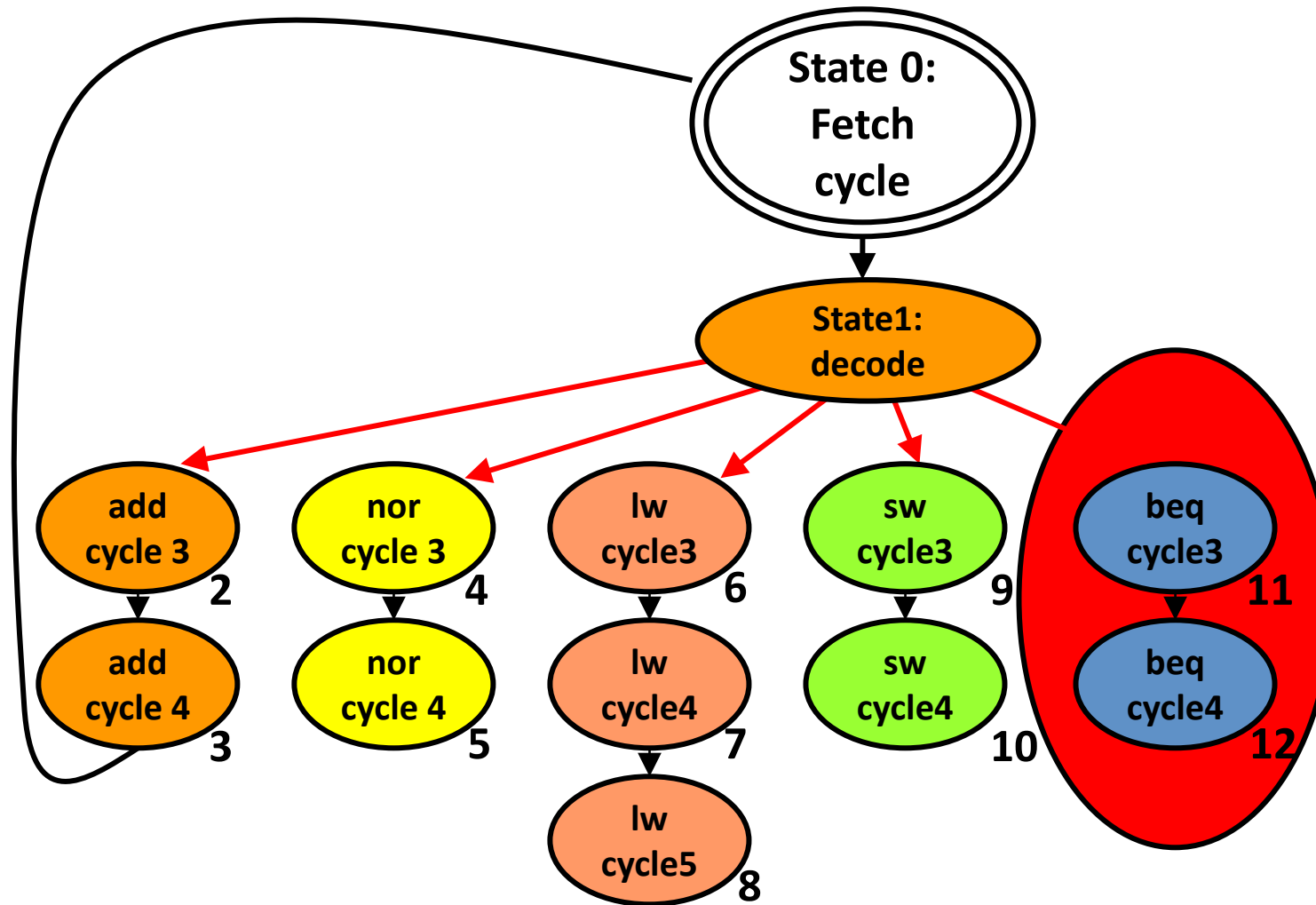
# Return to State 0: Fetch cycle to execute the next instruction




What do we need to do during BEQ?

# State 11: beq cycle 3


What will the control bits be?

Calculate target address for branch

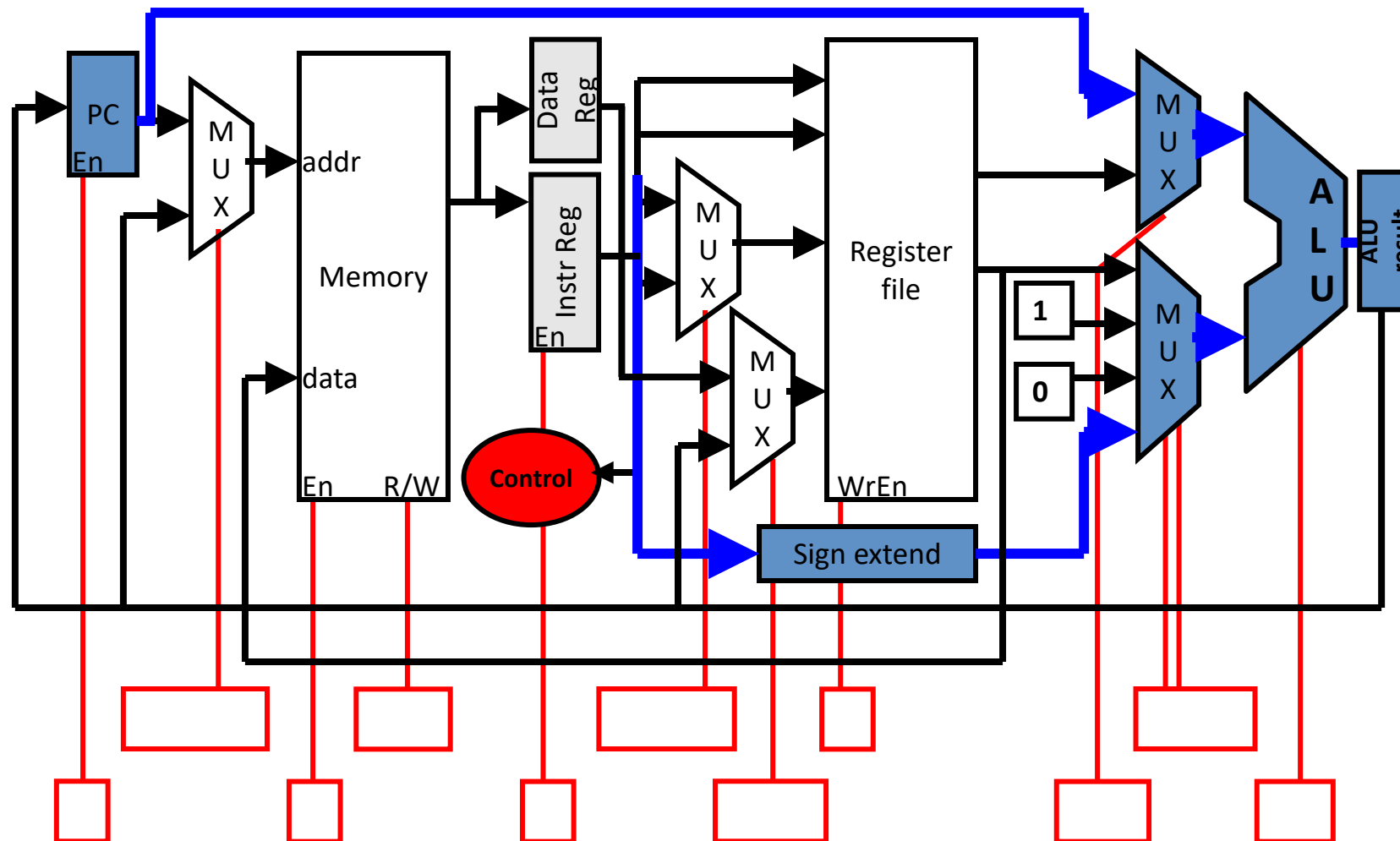


# State 11: beq cycle 3

Calculate target address for branch

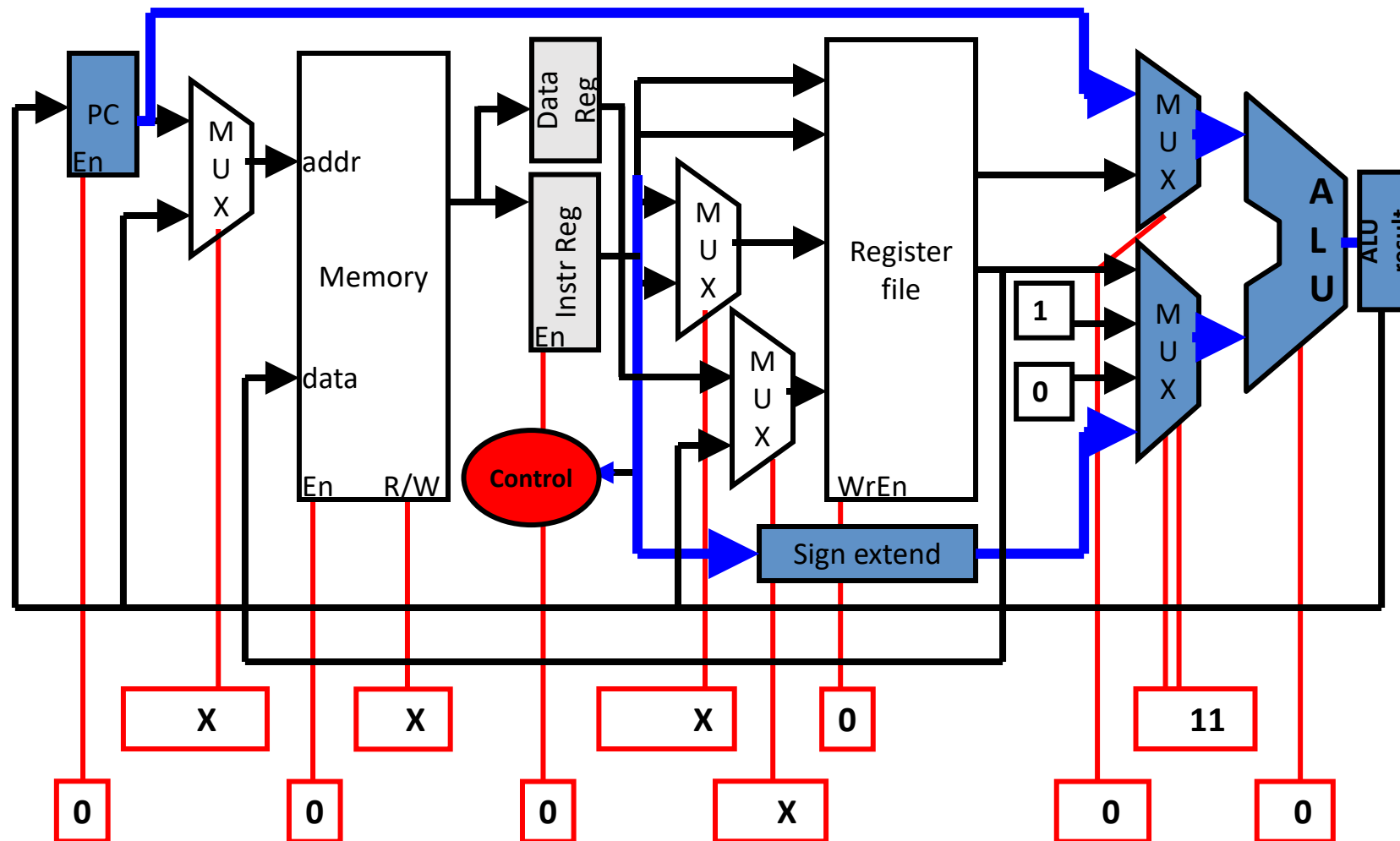


Control Rom (beq cycle 3)

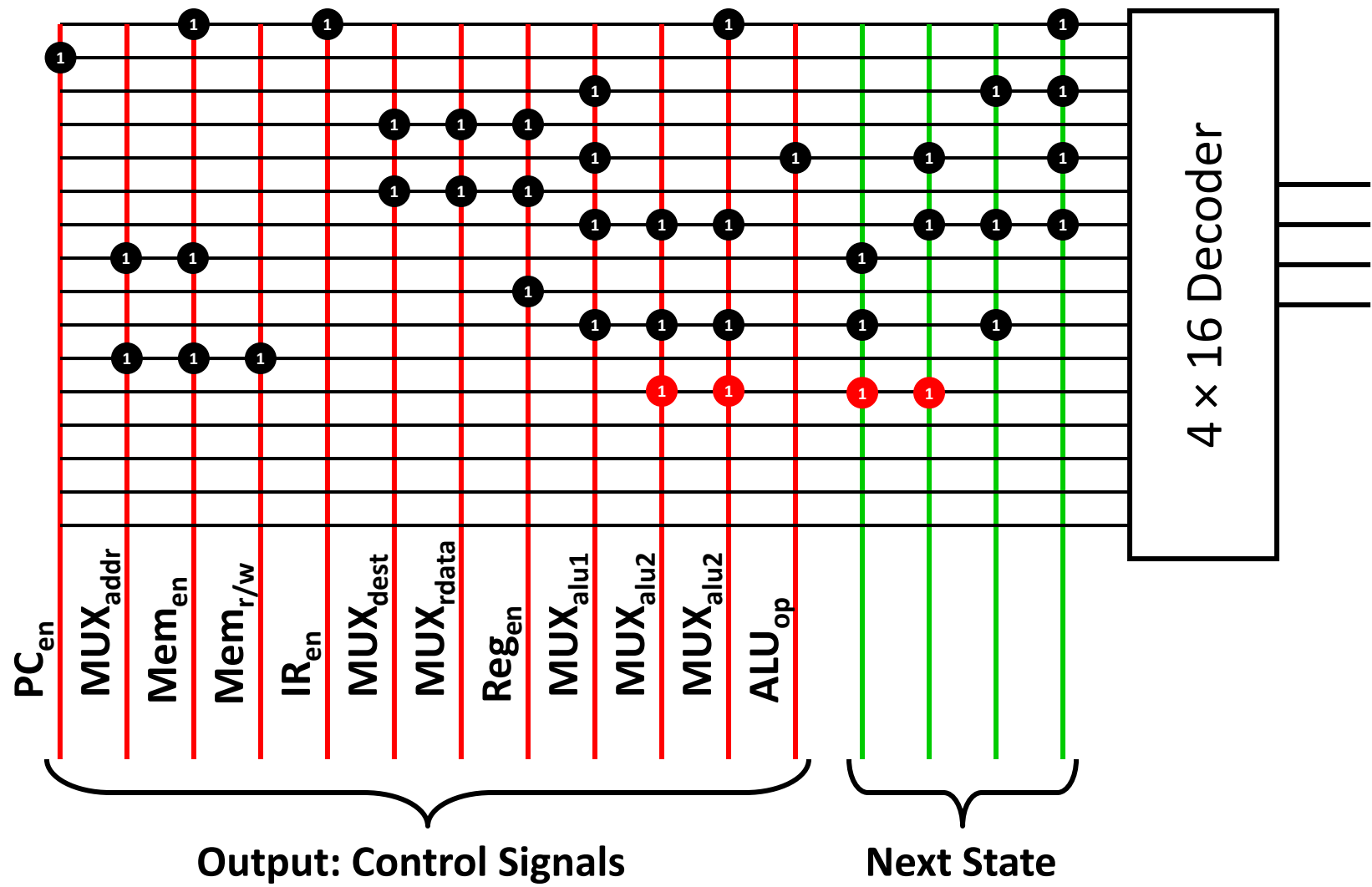
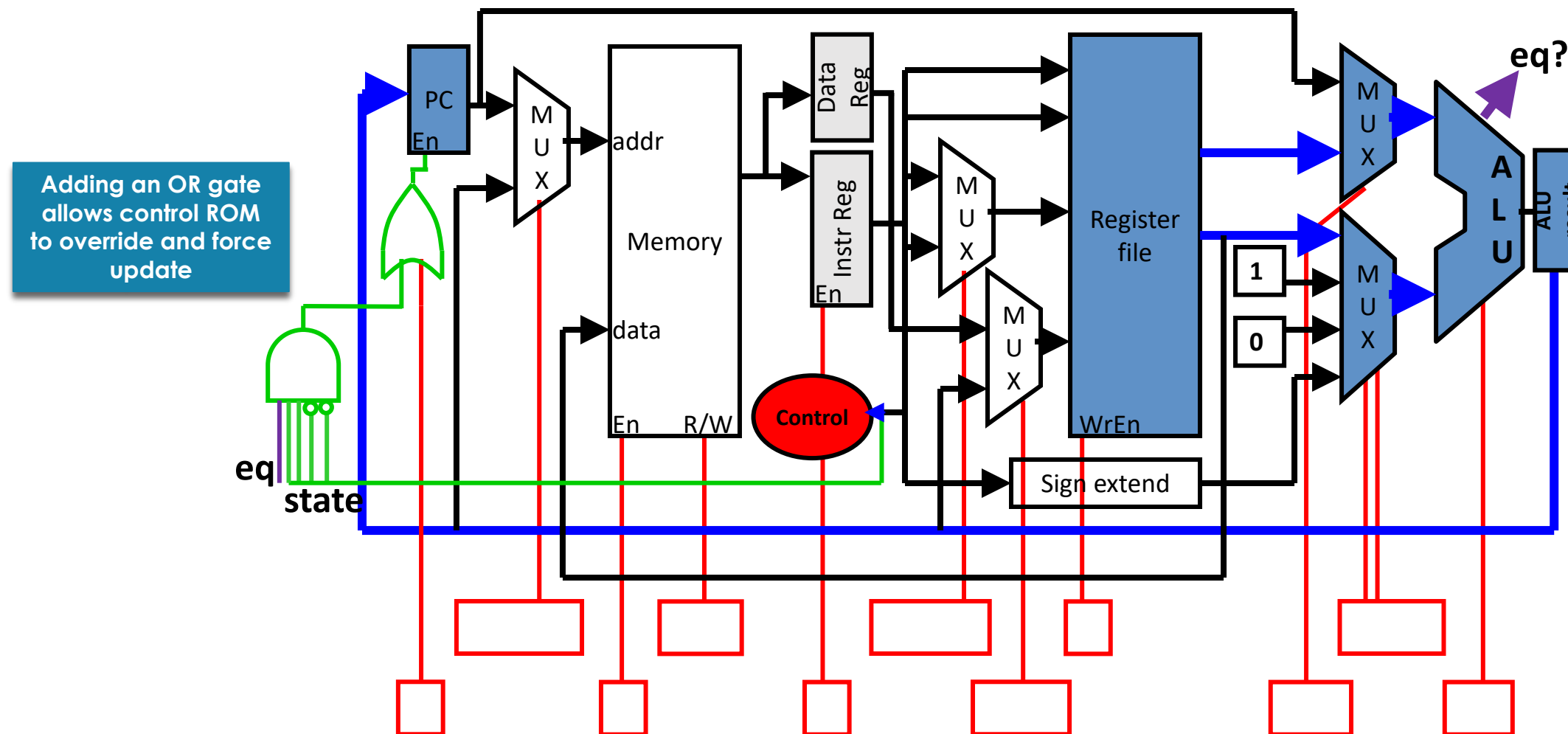
## State 12: beq cycle 4


**Write target address into PC**  
**if (data<sub>rega</sub> == data<sub>regb</sub>)**





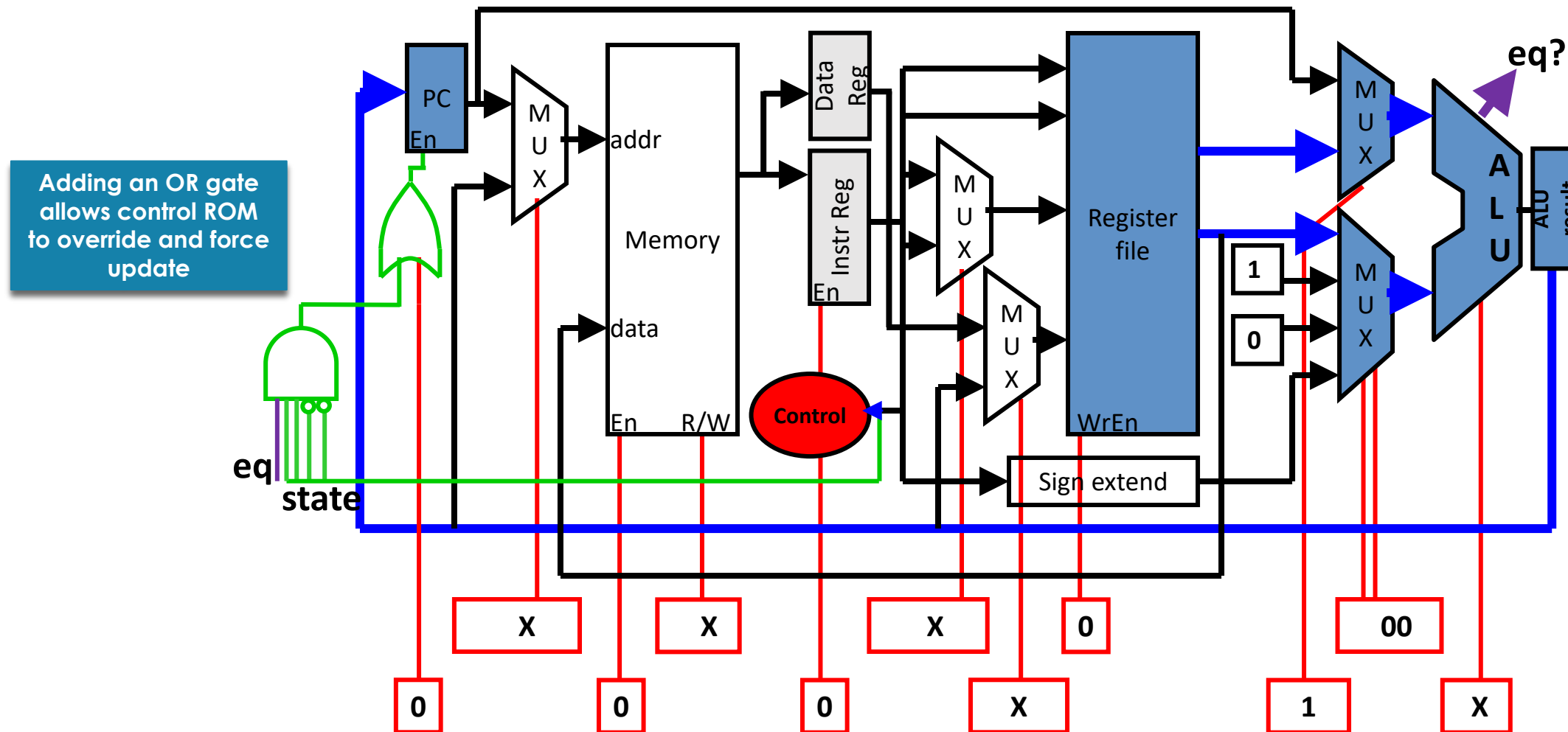
# State 12: beq cycle 4

Write target address into PC  
if ( $\text{data}_{\text{rega}} == \text{data}_{\text{regb}}$ )



Control Rom (beq cycle 4)

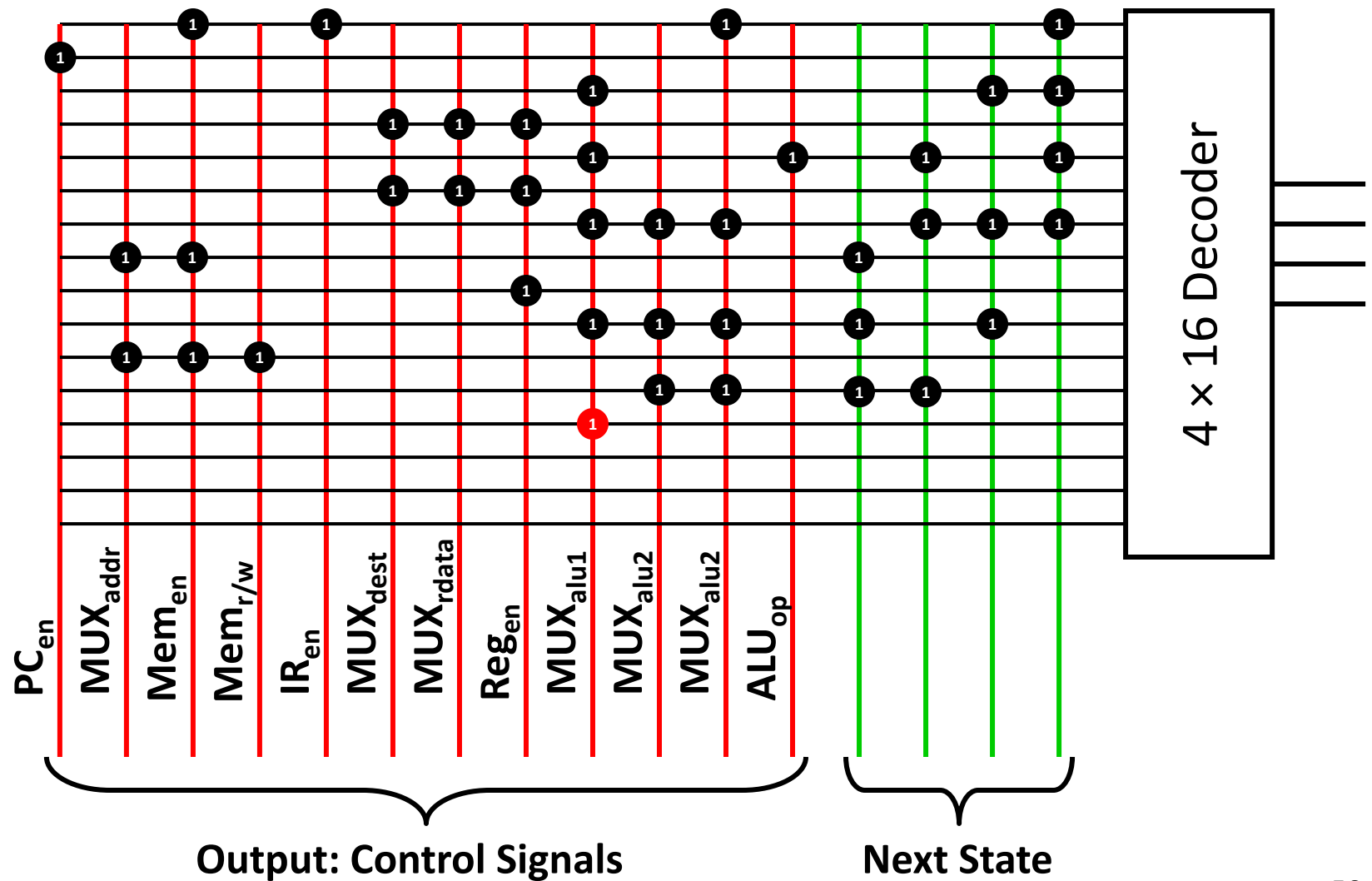

# Single vs Multi-cycle Performance

1 ns – Register File read/write time

2 ns – ALU/adder

2 ns – memory access

0 ns – MUX, PC access, sign extend, ROM

How many ns does SC take? MC?

1. Assuming the above delays, what is the best cycle time that the LC2k multi-cycle datapath could achieve? Single cycle?
2. Assuming the above delays, for a program consisting of 25 LW, 10 SW, 45 ADD, and 20 BEQ, which is faster?

# Single vs Multi-cycle Performance

1 ns – Register File read/write time

2 ns – ALU/adder

2 ns – memory access

0 ns – MUX, PC access, sign extend,  
ROM

1. Assuming the above delays, what is the best cycle time that the LC2k multi-cycle datapath could achieve? Single cycle?

$$\text{MC: } \text{MAX}(2, 1, 2, 2, 1) = 2\text{ns}$$

$$\text{SC: } 2 + 1 + 2 + 2 + 1 = 8\text{ ns}$$

2. Assuming the above delays, for a program consisting of 25 LW, 10 SW, 45 ADD, and 20 BEQ, which is faster?

$$\text{SC: } 100 \text{ cycles} * 8 \text{ ns} = 800 \text{ ns}$$

$$\text{MC: } (25*5 + 10*4 + 45*4 + 20*4)\text{cycles} * 2\text{ns} = 850 \text{ ns}$$



# Single and Multi-cycle performance

- Wait, multi-cycle is worse??
- For our ISA, most instructions take about the same time
- Multi-cycle shines when some instructions take much longer
- E.g. if we add a long latency instruction like multiply:
  - Let's say operation takes 10 ns, but could be split into 5 stages of 2 ns
  - SC: clock period = 16 ns, performance is 1600 ns
  - MC: clock period = 2 ns, performance is 850 ns

# Performance Metrics – Execution time

- What we really care about in a program is **execution time**
  - **Execution time** = total instructions executed X CPI x clock period
  - The "Iron Law" of performance
- CPI = **average** number of clock **cycles per instruction** *for an application*
- To calculate multi-cycle CPI we need:
  - Cycles necessary for each type of instruction
  - Mix of instructions executed in the application (dynamic instruction execution profile)

What are the units of (instructions executed x CPI x clock period)?

# Datapath Summary


- Single-cycle processor
  - CPI = 1 (by definition)
  - clock period =  $\sim 10$  ns
- Multi-cycle processor
  - CPI =  $\sim 4.25$
  - clock period =  $\sim 2$  ns
- Better design:
  - CPI = 1
  - clock period =  $\sim 2$  ns
- How??
  - Work on multiple instructions at the same time

# Pipelining


- Want to execute an instruction?
  - Build a processor (multi-cycle)
  - Find instructions
  - Line up instructions (1, 2, 3, ...)
  - Overlap execution
    - Cycle #1: Fetch 1
    - Cycle #2: Decode 1      Fetch 2
    - Cycle #3: ALU 1      Decode 2      Fetch 3
    - .....
  - This is called pipelining instruction execution.
  - Used extensively for the first time on IBM 360 (1960s).
  - CPI approaches 1.



# Pipelining

 

# Pipelining

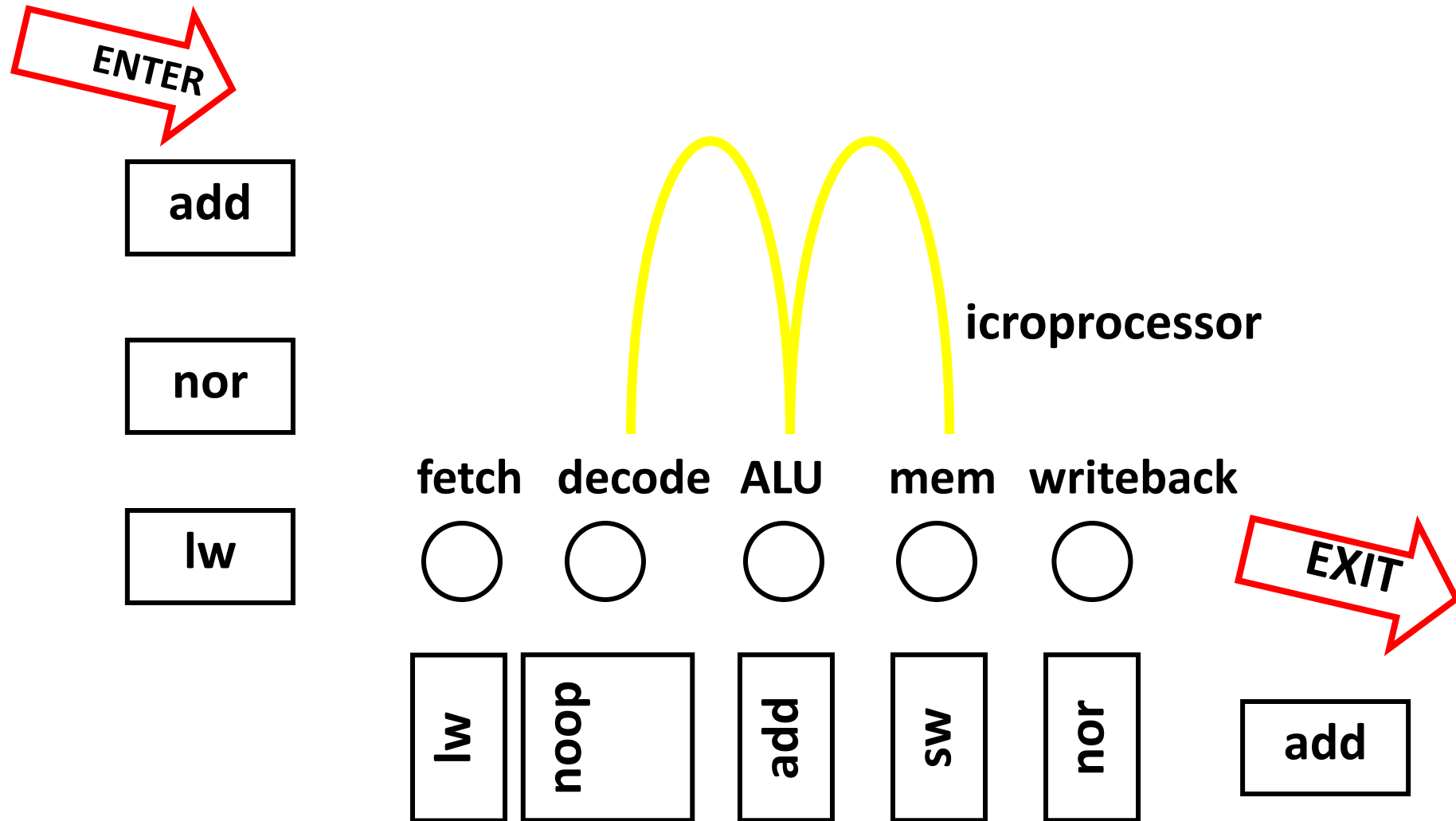


# Pipelined implementation of LC2K

- Break the execution of the instruction into cycles.
  - Similar to the multi-cycle datapath
- Design a separate datapath **stage** for the execution performed during each cycle.
  - Build **pipeline registers** to communicate between the stages.
  - Whatever is on the left gets written onto the right during the next cycle
  - Kinda like the **Instruction Register** in our multi-cycle design, but we'll need one for each stage



# Our new pipelined datapath

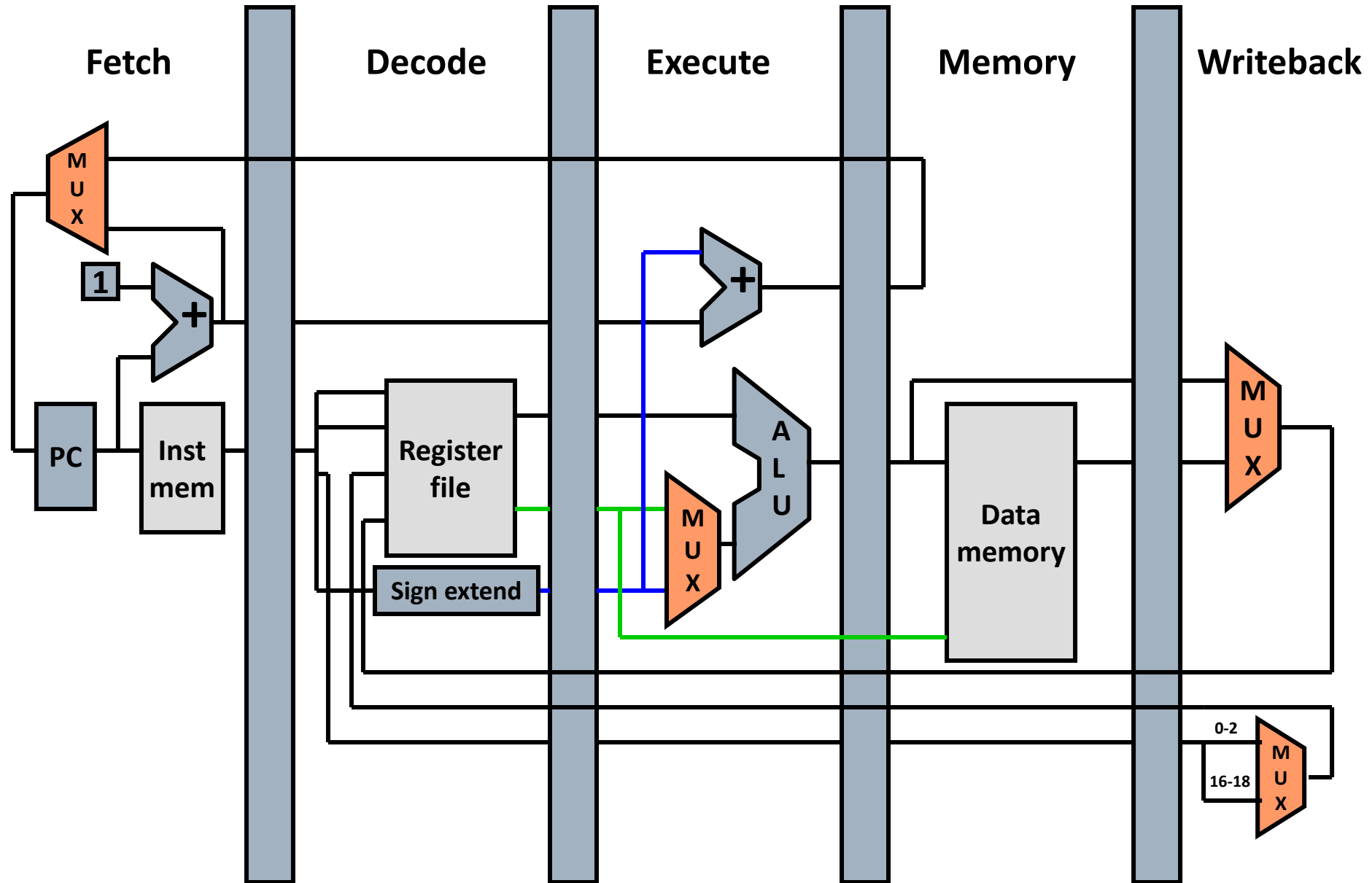

# Next time

- More pipelining

